



Introduction to the Amplifier


Nikolay Nikolaev

(nanikolaev@itmo.ru)

Nikolai Poliakov

(polyakov_n_a@itmo.ru)


Introduction to the Amplifier

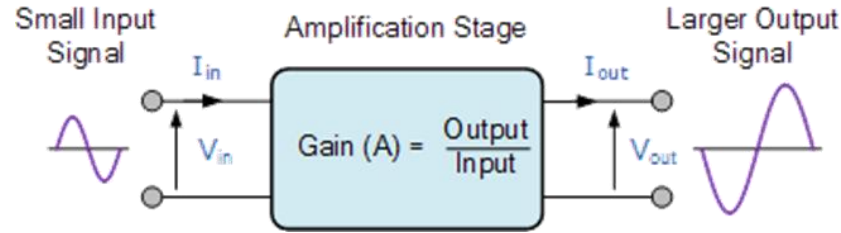

$$\text{Voltage Gain } (A_v) = \frac{\text{Output Voltage}}{\text{Input Voltage}} = \frac{V_{out}}{V_{in}}$$

$$\text{Current Gain } (A_i) = \frac{\text{Output Current}}{\text{Input Current}} = \frac{I_{out}}{I_{in}}$$


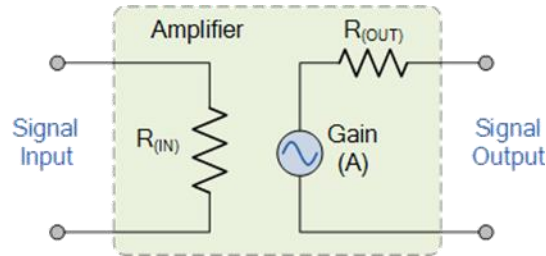
$$\text{Power Gain } (A_p) = A_v \times A_i$$



Voltage Gain in dB: $a_v = 20 \log(A_v)$


Current Gain in dB: $a_i = 20 \log(A_i)$

Power Gain in dB: $a_p = 10 \log(A_p)$

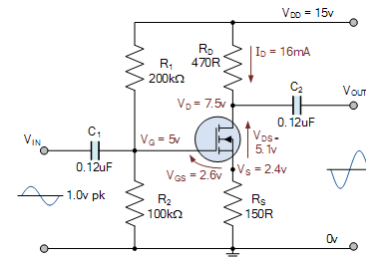
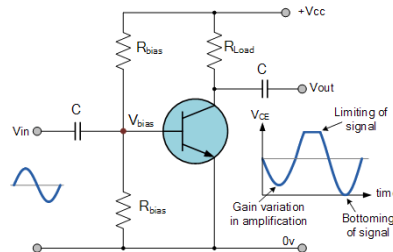


Type of Signal	Type of Configuration	Classification	Frequency of Operation
Small Signal	Common Emitter	Class A Amplifier	Direct Current (DC)
Large Signal	Common Base	Class B Amplifier	Audio Frequencies (AF)
	Common Collector	Class AB Amplifier	Radio Frequencies (RF)
		Class C Amplifier	VHF, UHF and SHF Frequencies



- ✓ The amplifiers gain, (A) should remain constant for varying values of input signal.
- ✓ Gain is not be affected by frequency. Signals of all frequencies must be amplified by exactly the same amount.
- ✓ The amplifiers gain must not add noise to the output signal. It should remove any noise that is already exists in the input signal.
- ✓ The amplifiers gain should not be affected by changes in temperature giving good temperature stability.
- ✓ The gain of the amplifier must remain stable over long periods of time.


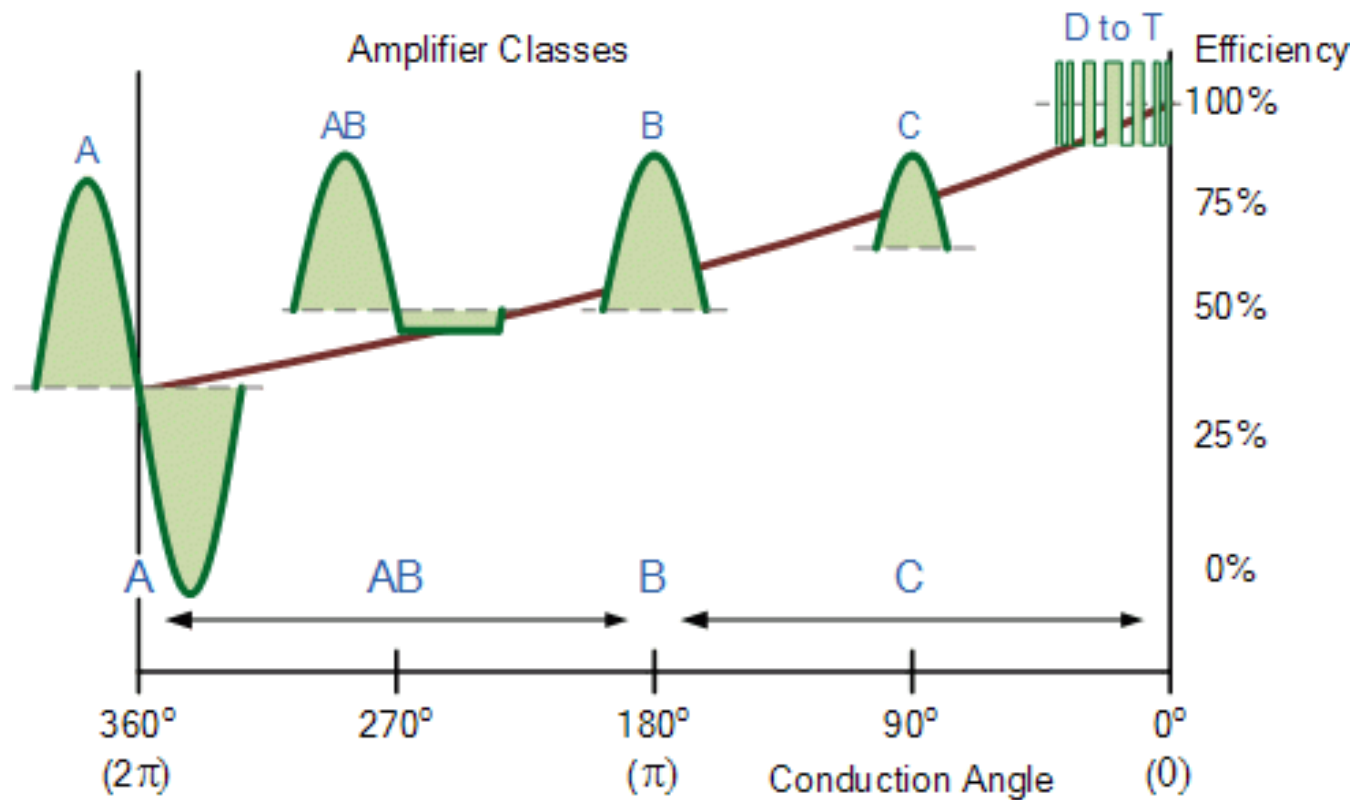




Class A Amplifier

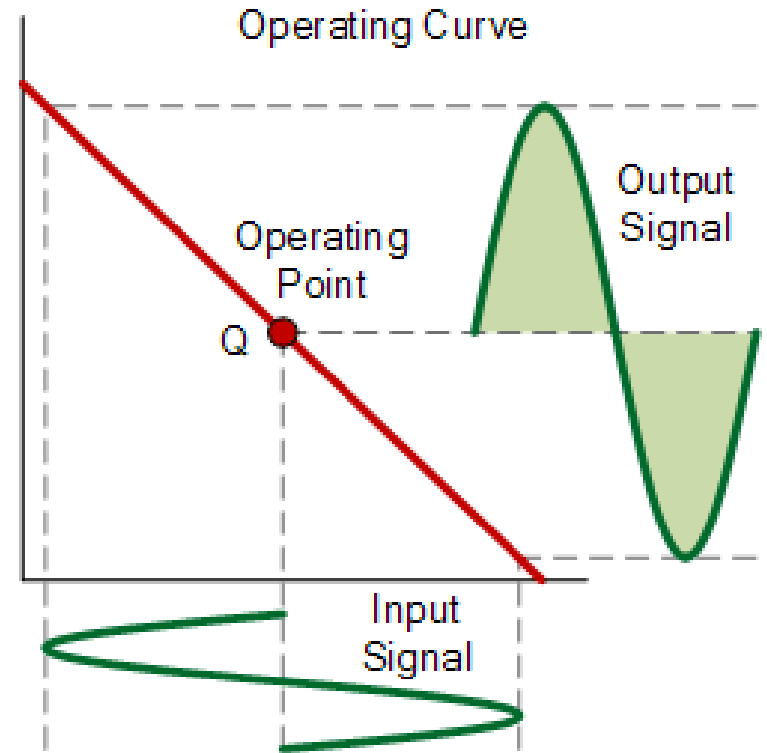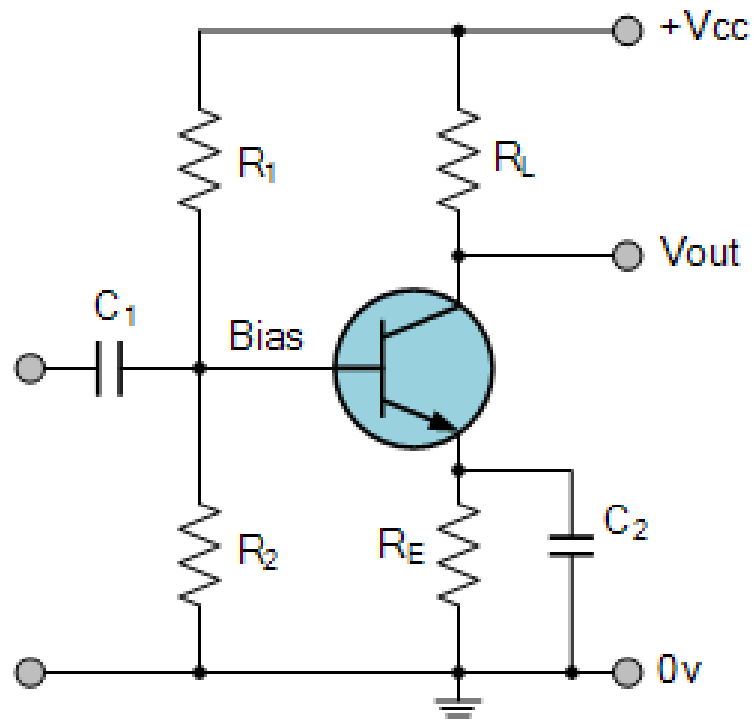

Class B Amplifier

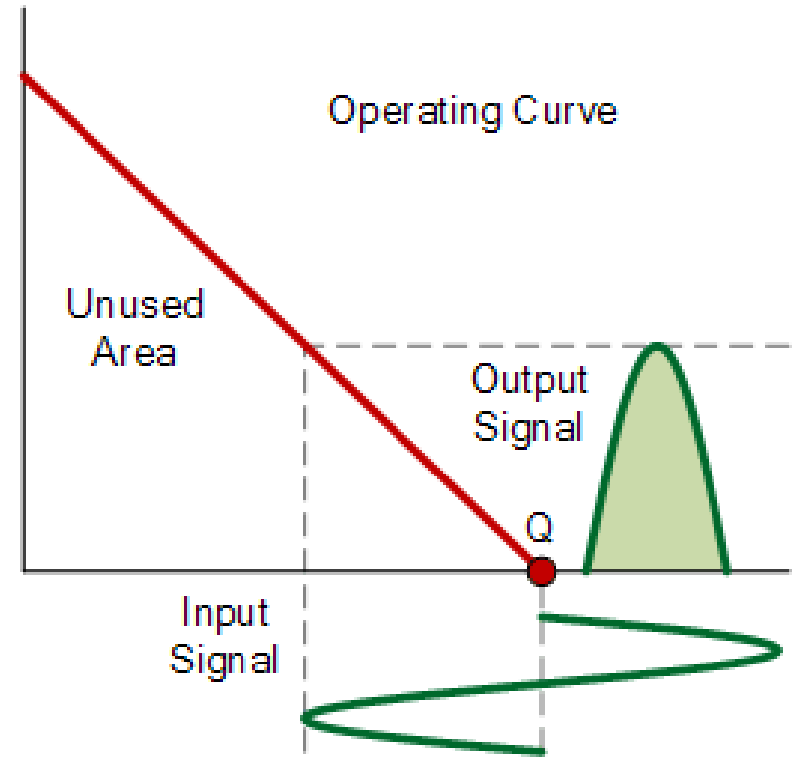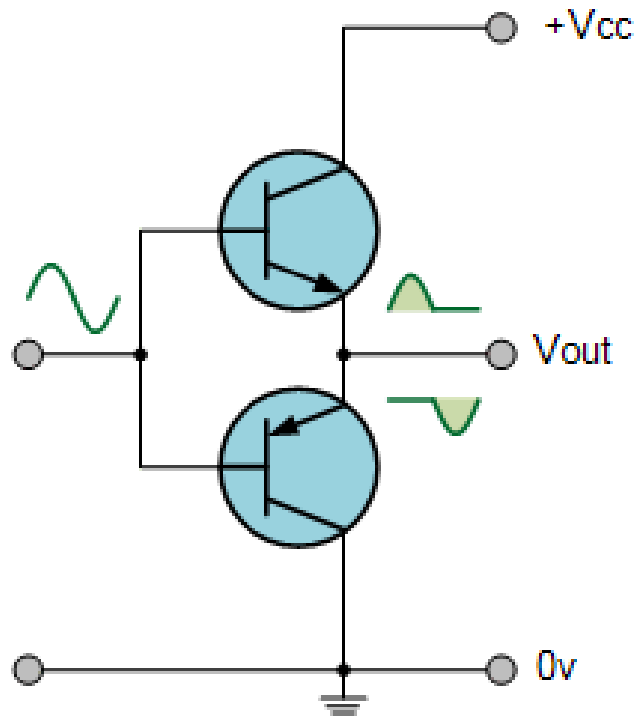

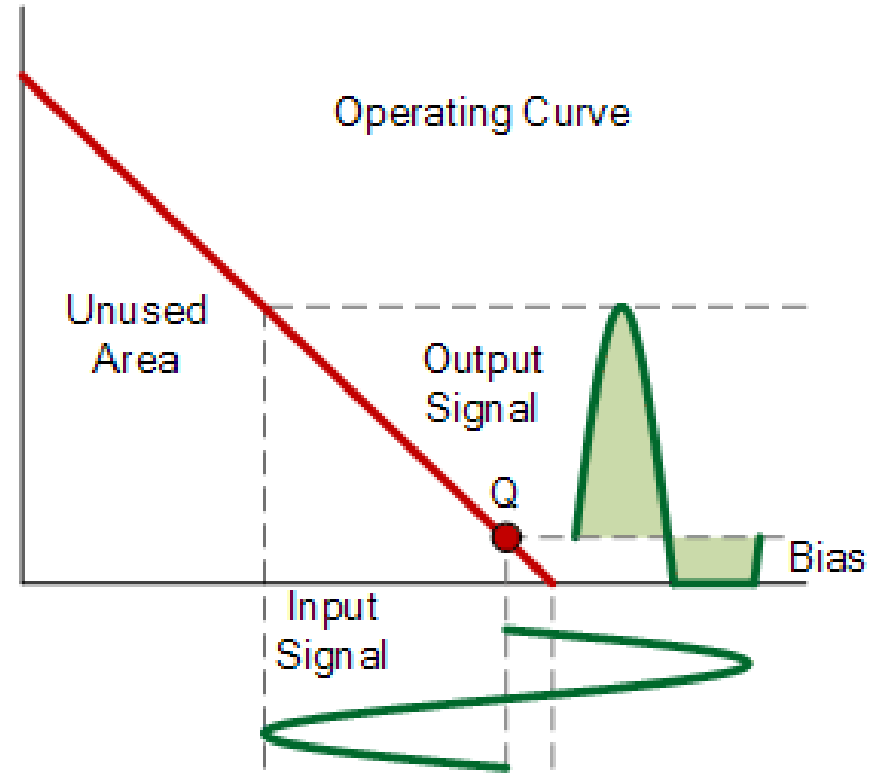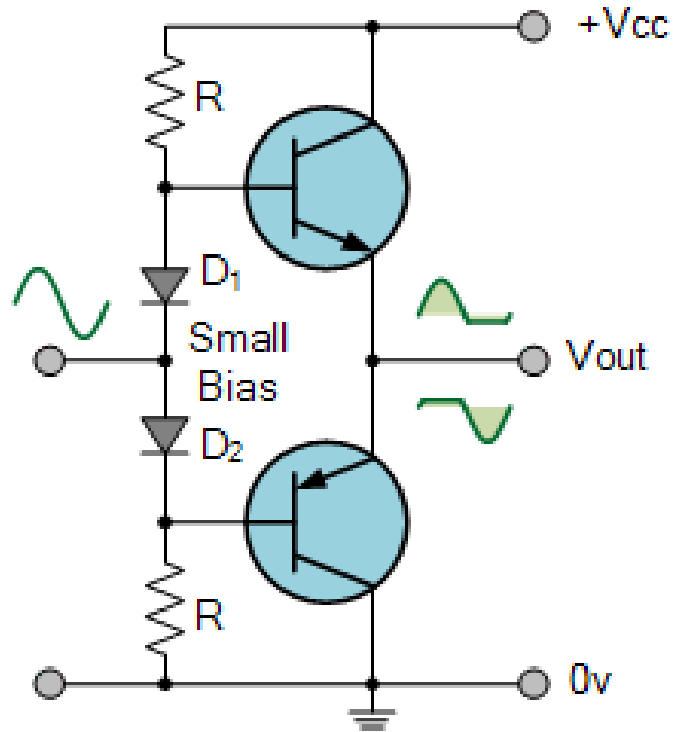

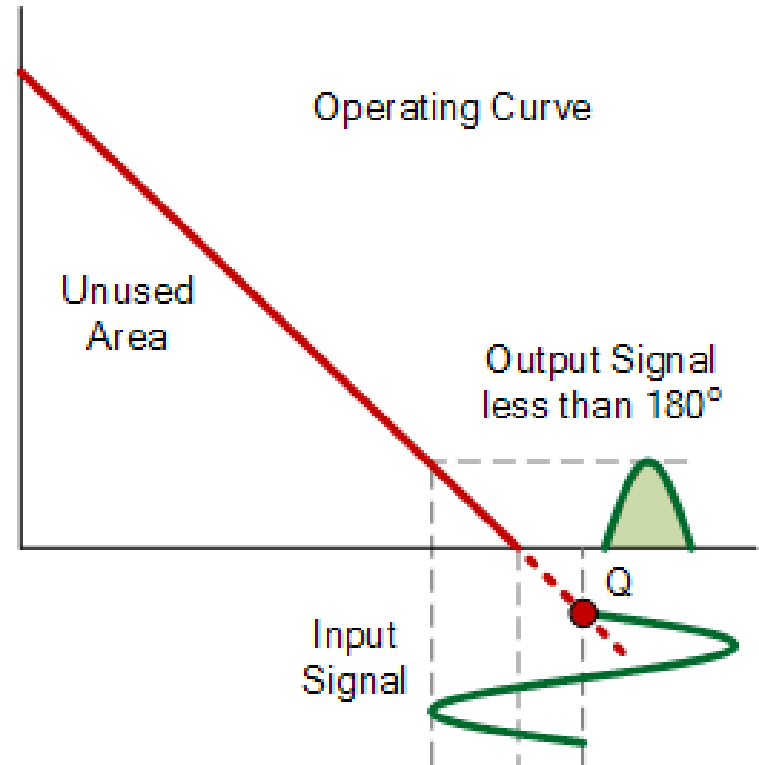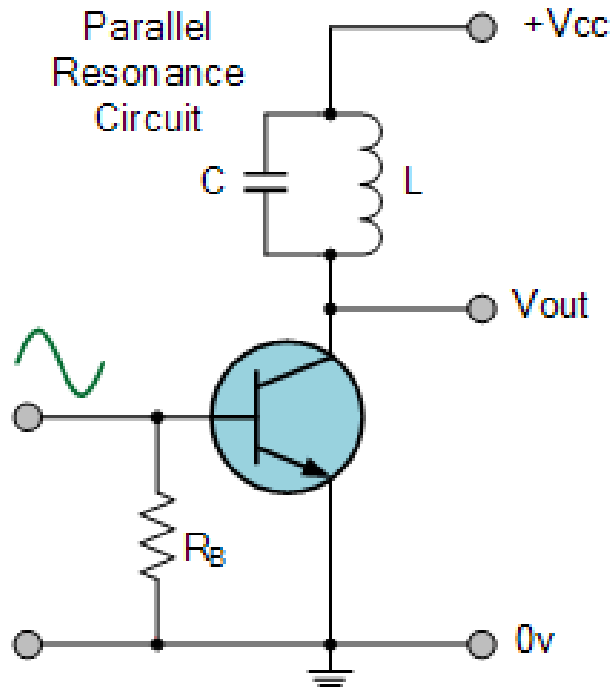


- Class D Amplifier – A Class D audio amplifier is basically a non-linear switching amplifier or PWM amplifier. Class-D amplifiers theoretically can reach 100% efficiency, as there is no period during a cycle where the voltage and current waveforms overlap as current is drawn only through the transistor that is on.
- Class F Amplifier – Class-F amplifiers boost both efficiency and output by using harmonic resonators in the output network to shape the output waveform into a square wave. Class-F amplifiers are capable of high efficiencies of more than 90% if infinite harmonic tuning is used.
- Class G Amplifier – Class G offers enhancements to the basic class AB amplifier design. Class G uses multiple power supply rails of various voltages and automatically switches between these supply rails as the input signal changes. This constant switching reduces the average power consumption, and therefore power loss caused by wasted heat.
- Class I Amplifier – The class I amplifier has two sets of complementary output switching devices arranged in a parallel push-pull configuration with both sets of switching devices sampling the same input waveform. One device switches the positive half of the waveform, while the other switches the negative half similar to a class B amplifier. With no input signal applied, or when a signal reaches the zero crossing point, the switching devices are both turned ON and OFF simultaneously with a 50% PWM duty cycle cancelling out any high frequency signals.


- Class S Amplifier – A class S power amplifier is a non-linear switching mode amplifier similar in operation to the class D amplifier. The class S amplifier converts analogue input signals into digital square wave pulses by a delta-sigma modulator, and amplifies them to increase the output power before finally being demodulated by a band pass filter. As the digital signal of this switching amplifier is always either fully “ON” or “OFF” (theoretically zero power dissipation), efficiencies reaching 100% are possible.
- Class T Amplifier – The class T amplifier is another type of digital switching amplifier design. Class T amplifiers are starting to become more popular these days as an audio amplifier design due to the existence of digital signal processing (DSP) chips and multi-channel surround sound amplifiers as it converts analogue signals into digital pulse width modulated (PWM) signals for amplification increasing the amplifiers efficiency. Class T amplifier designs combine both the low distortion signal levels of class AB amplifier and the power efficiency of a class D amplifier.

Amplifier Class	Description	Conduction Angle
Class-A	Full cycle 360° of Conduction	$\theta = 2\pi$
Class-B	Half cycle 180° of Conduction	$\theta = \pi$
Class-AB	Slightly more than 180° of conduction	$\pi < \theta < 2\pi$
Class-C	Slightly less than 180° of conduction	$\theta < \pi$
Class-D to T	ON-OFF non-linear switching	$\theta = 0$

Power Amplifier Classes

Class	A	B	C	AB
Conduction Angle	360°	180°	Less than 90°	180 to 360°
Position of the Q-point	Centre Point of the Load Line	Exactly on the X-axis	Below the X-axis	In between the X-axis and the Centre Load Line
Overall Efficiency	Poor 25 to 30%	Better 70 to 80%	Higher than 80%	Better than A but less than B 50 to 70%
Signal Distortion	None if Correctly Biased	At the X-axis Crossover Point	Large Amounts	Small Amounts

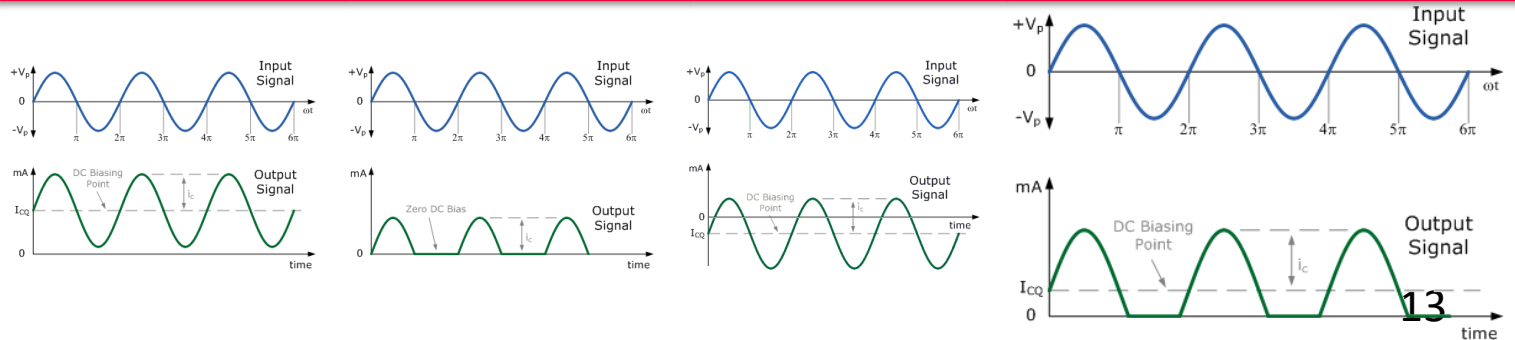

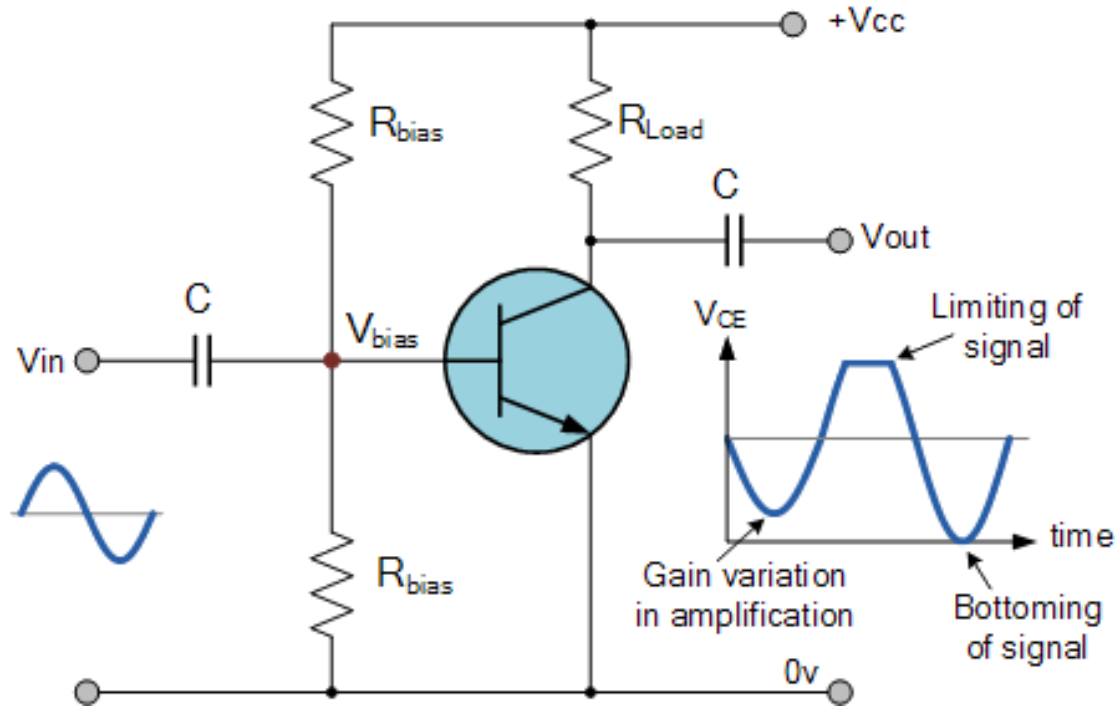


Distortion of the output signal waveform may occur because:


- ✓ Amplification may not be taking place over the whole signal cycle due to incorrect biasing levels.
- ✓ The input signal may be too large, causing the amplifiers transistors to be limited by the supply voltage.
- ✓ The amplification may not be a linear signal over the entire frequency range of inputs.

Distortion of the output signal waveform may occur because:

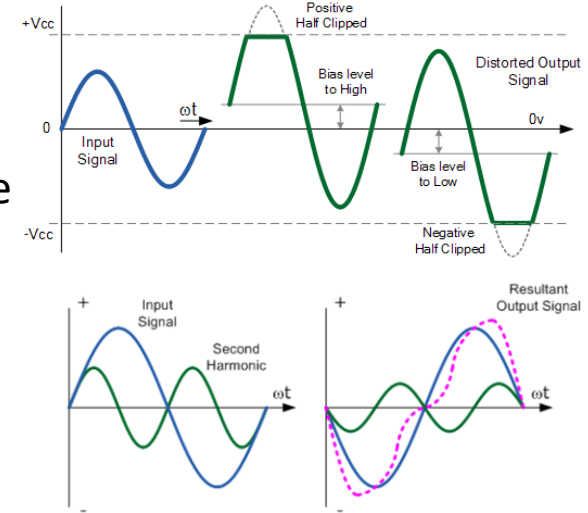- ✓ Amplification may not be taking place over the whole signal cycle due to incorrect biasing levels.
- ✓ The input signal may be too large, causing the amplifiers transistors to be limited by the supply voltage.
- ✓ The amplification may not be a linear signal over the entire frequency range of inputs.




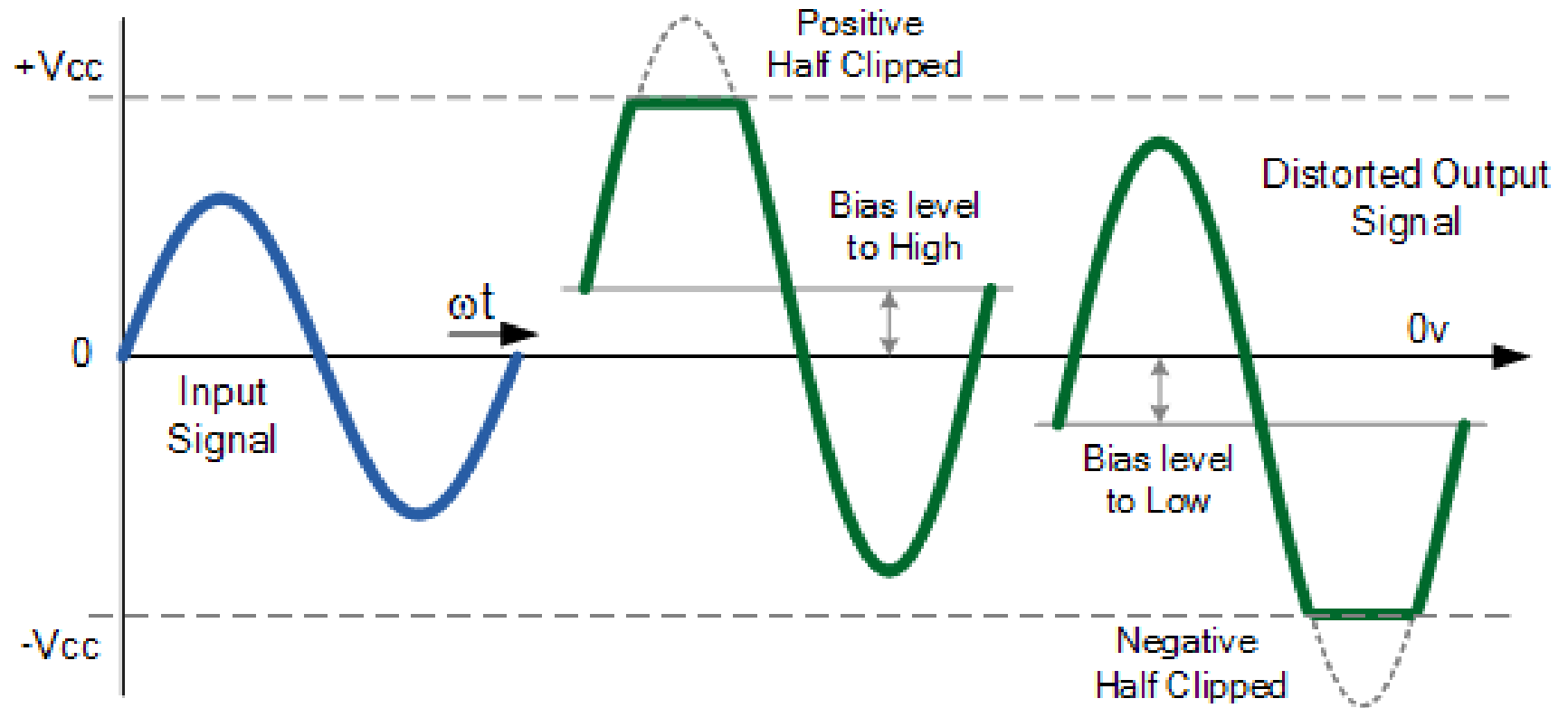This means then that during the amplification process of the signal waveform, some form of Amplifier Distortion has occurred.




itmo



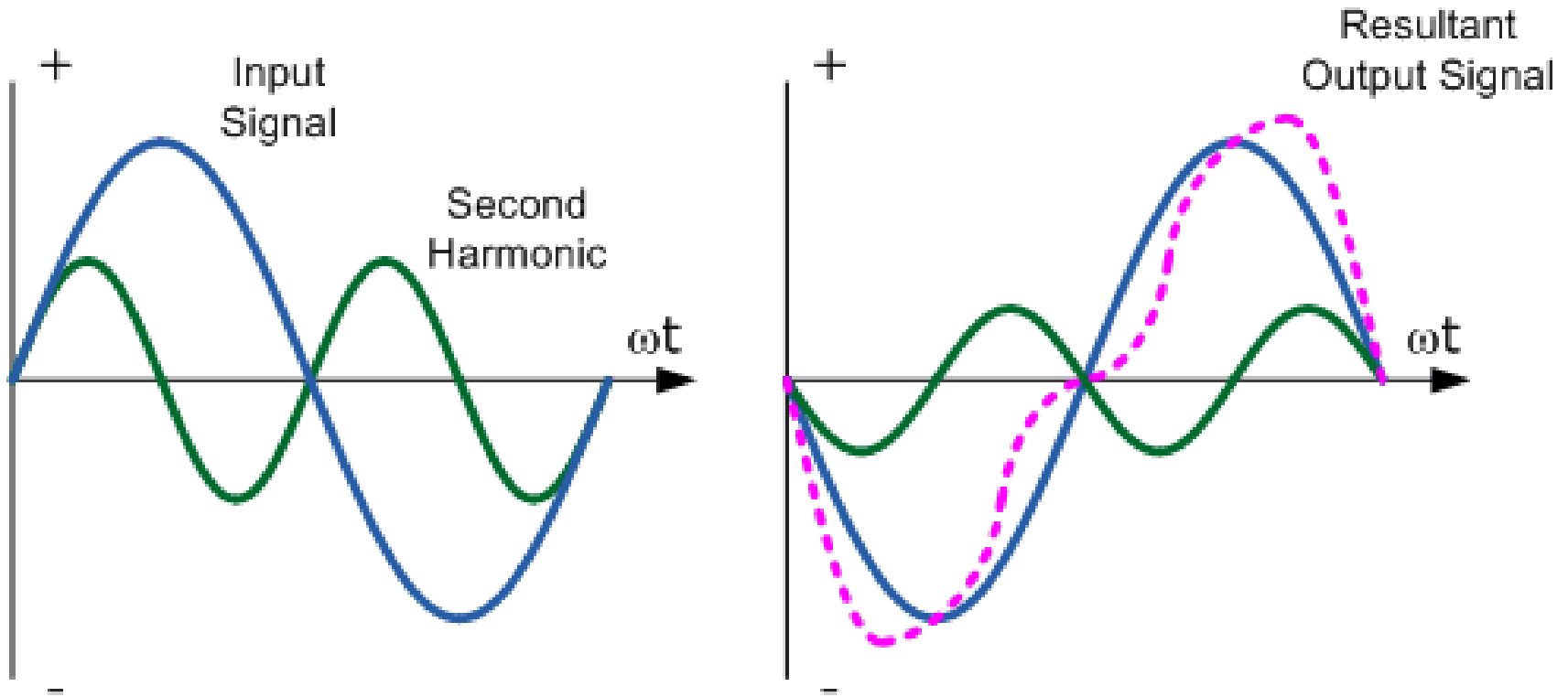

Phase Distortion due to Delay

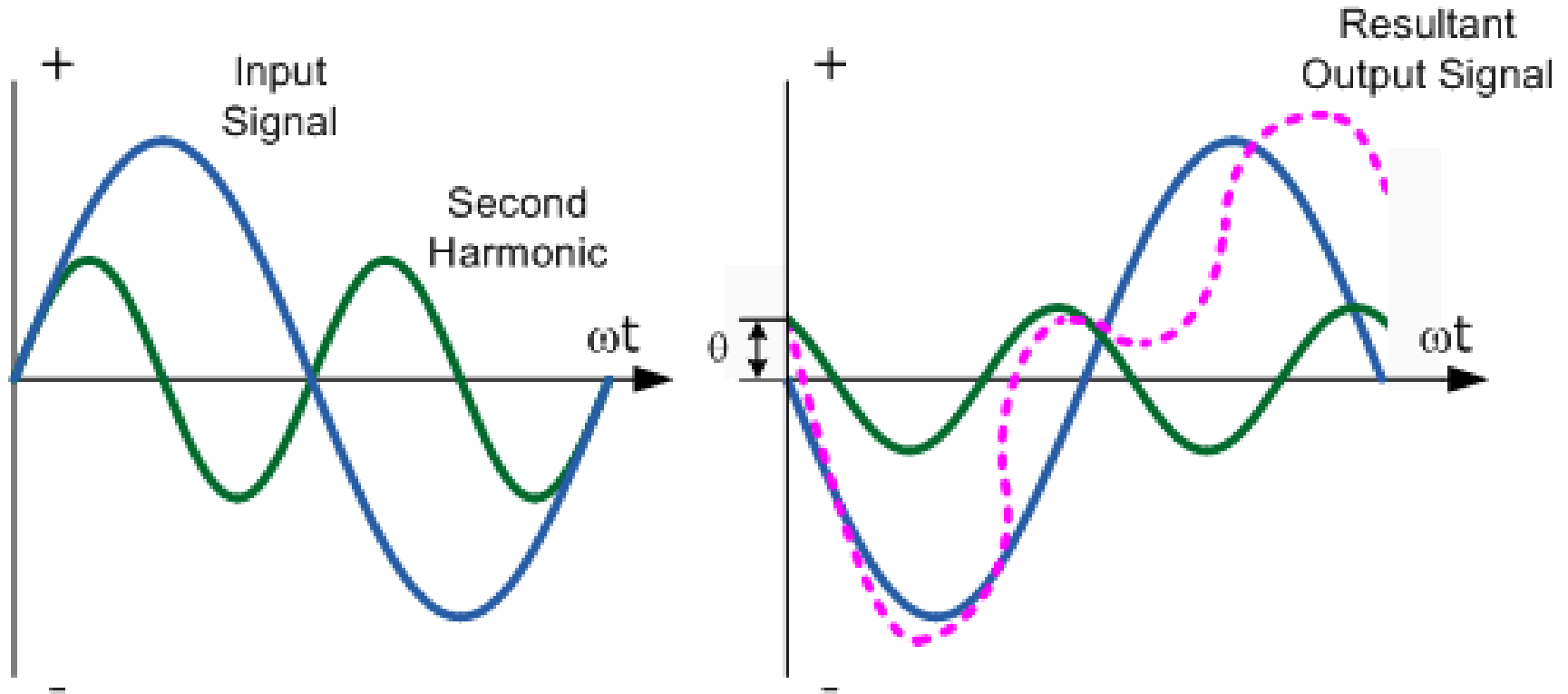


The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a bright purple color, creating a modern, abstract aesthetic.

iTMO

Common Emitter Amplifier

Common Emitter Amplifier

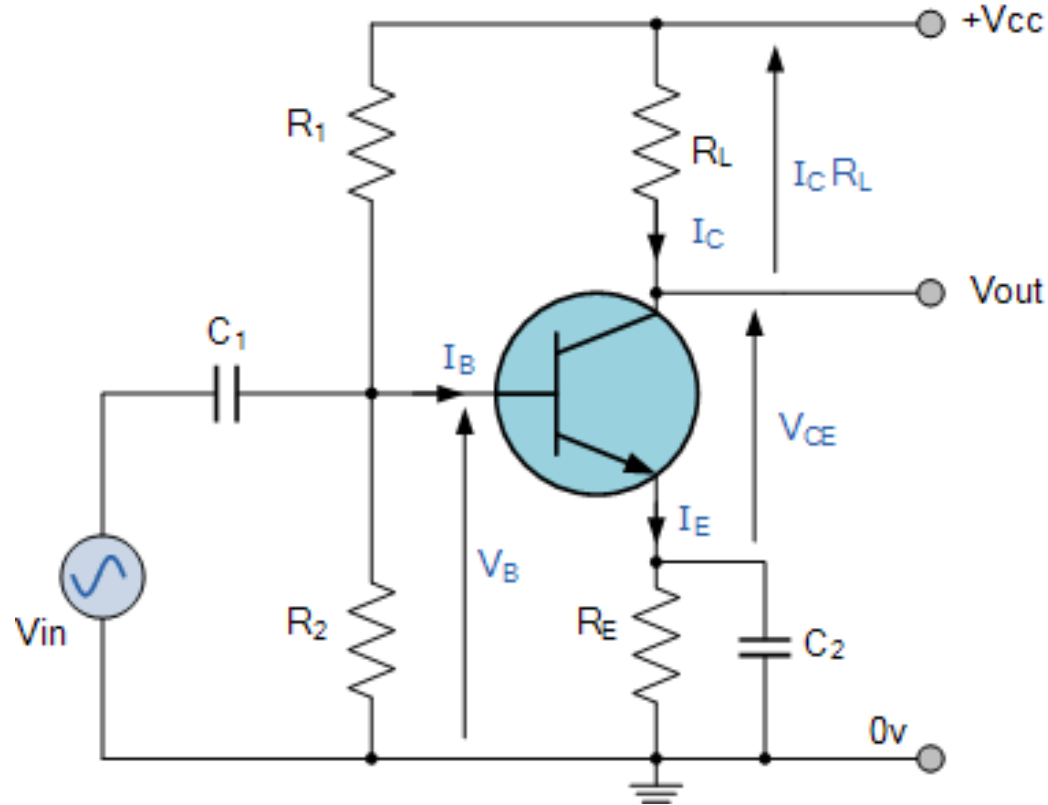

If


$$V_{CC} = 12\text{ V}$$

$$V_{RE} = 1\text{ V}$$

$$R_L = 1200\ \Omega$$

$$\beta = 100$$

Common Emitter Amplifier

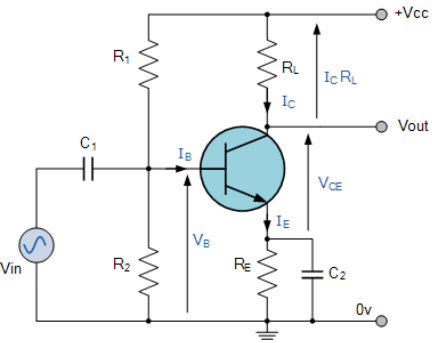

If

$$V_{CC} = 12\text{ V}$$

$$V_{RE} = 1\text{ V}$$

$$R_L = 1200\ \Omega$$

Load line

$$V_{CC} = V_{CE} + I_C R_L + V_{RE}$$


Saturation (A)

$$I_{Cmax} = \frac{V_{CE} - V_{RE}}{R_L} = \frac{12 - 1}{1200} = 9,2\text{ mA}$$


Cut-off (B)

$$I_C = 0, \Rightarrow V_{RE} = 0\text{ V}$$

$$V_{CE} = V_{CC}$$

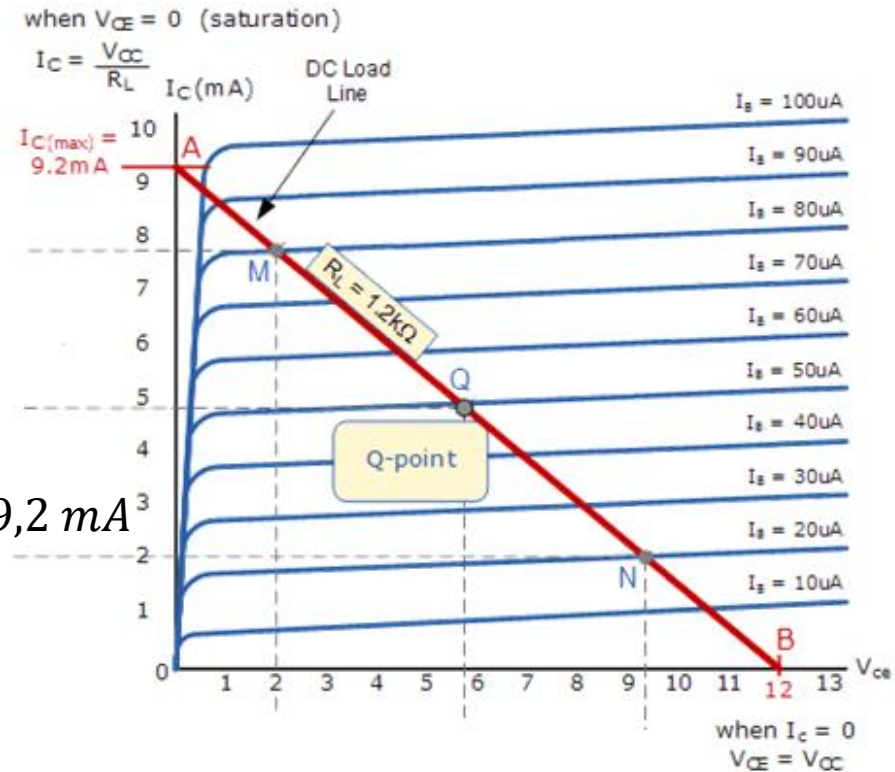

Common Emitter Amplifier

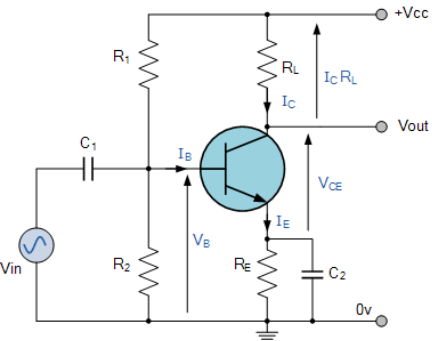

If

$$V_{CC} = 12\text{ V}$$

$$V_{RE} = 1\text{ V}$$

$$R_L = 1200\ \Omega$$


Q-point

$$I_{CQ} = \frac{V_{CC} - V_{RE}/2}{R_L}$$



$$I_{CQ} = \frac{12 - 1/2}{1200} = 4,58\text{ mA}$$

$$I_C = \beta * I_B \Rightarrow I_B = \frac{I_C}{\beta}$$
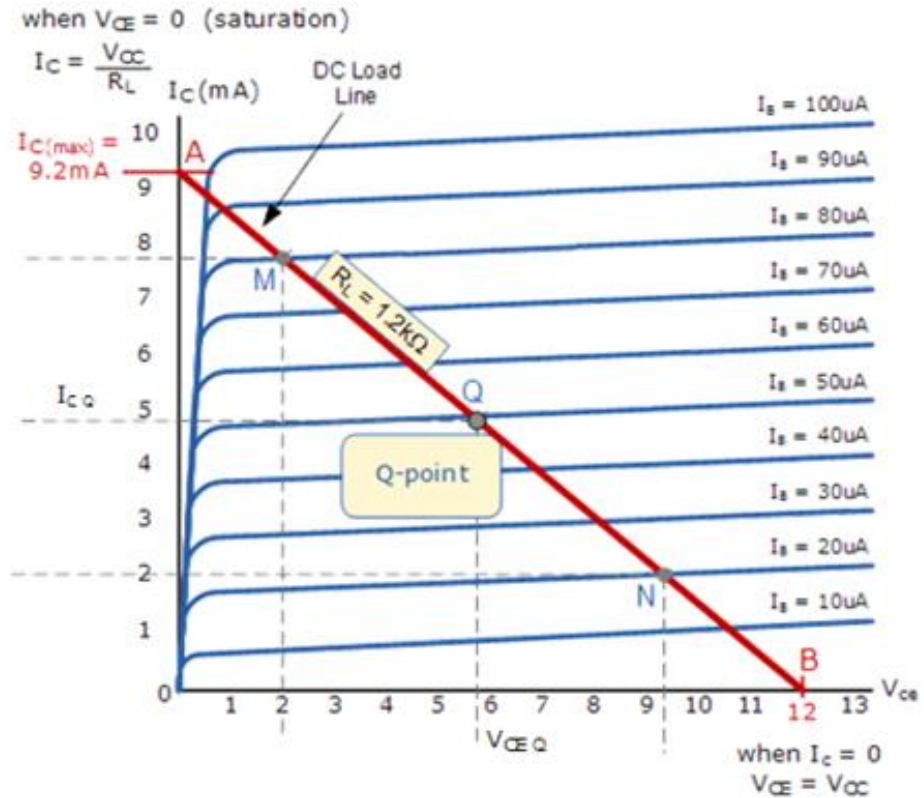
$$I_B = \frac{4,58}{100} = 45,8\ \mu\text{A}$$



Common Emitter Amplifier

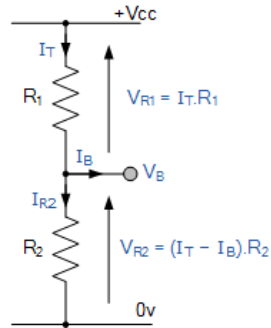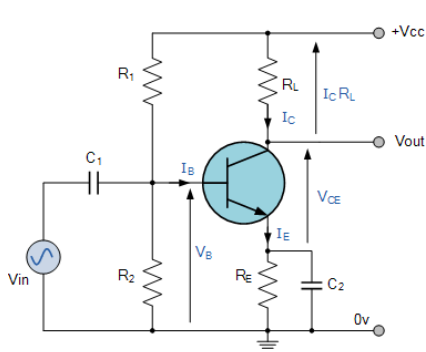


$$V_{R2} = V_{BE} + V_{RE}$$

$$I_{R2} * R_2 = V_{BE} + V_{RE}$$




$$I_{R2} \geq 10 * I_B$$

$$10I_B * R_2 = V_{BE} + V_{RE}$$
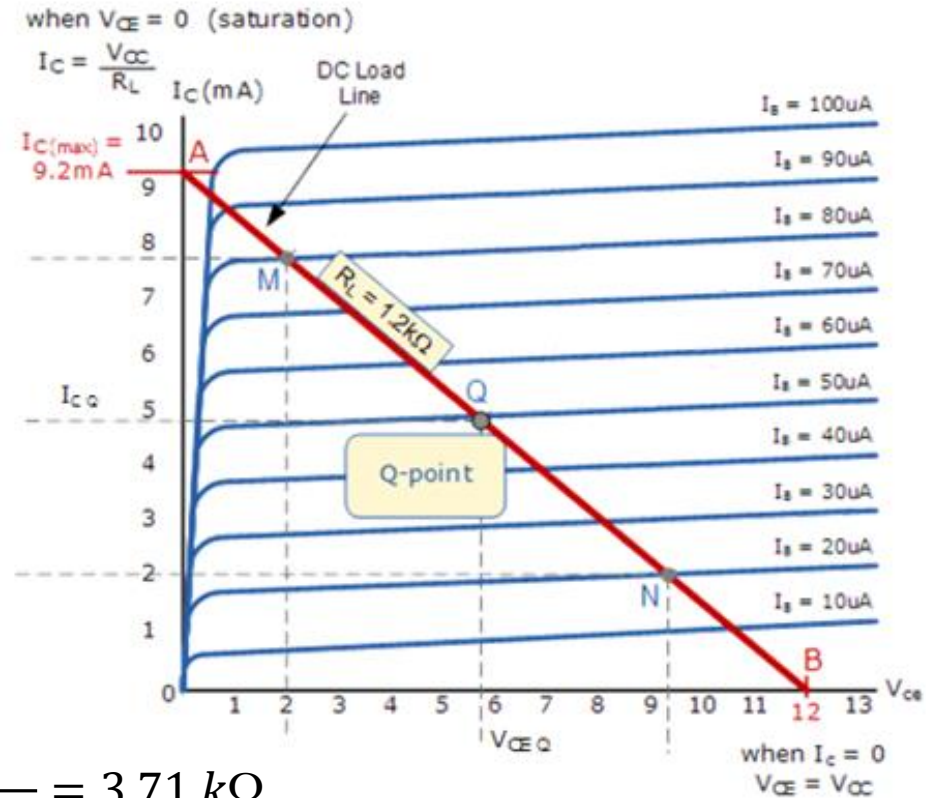
$$R_2 = \frac{V_{BE} + V_{RE}}{10I_B} = \frac{0.7 + 1}{10 * 45.8 * 10^{-6}} = 3,71 \text{ k}\Omega$$




Common Emitter Amplifier

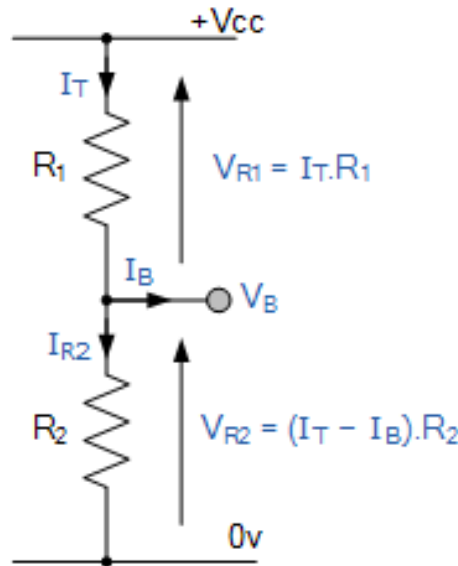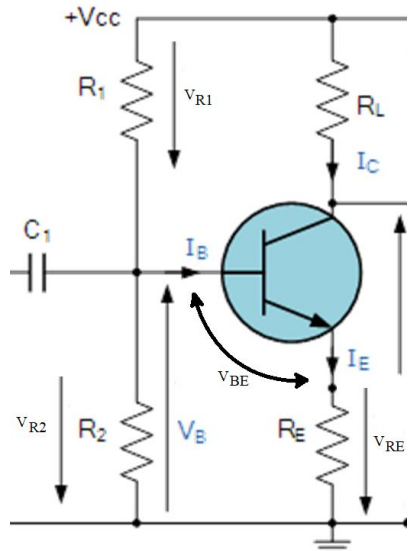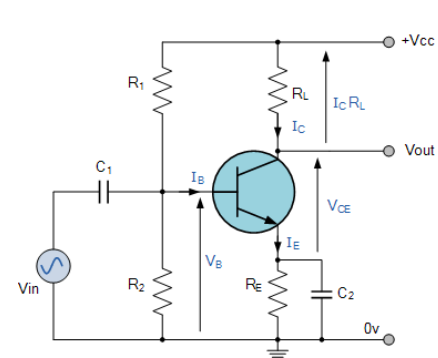




$$I_{R2} \geq 10 * I_B$$

$$I_{R1} \geq I_{R2} + I_B = 11 * I_B$$
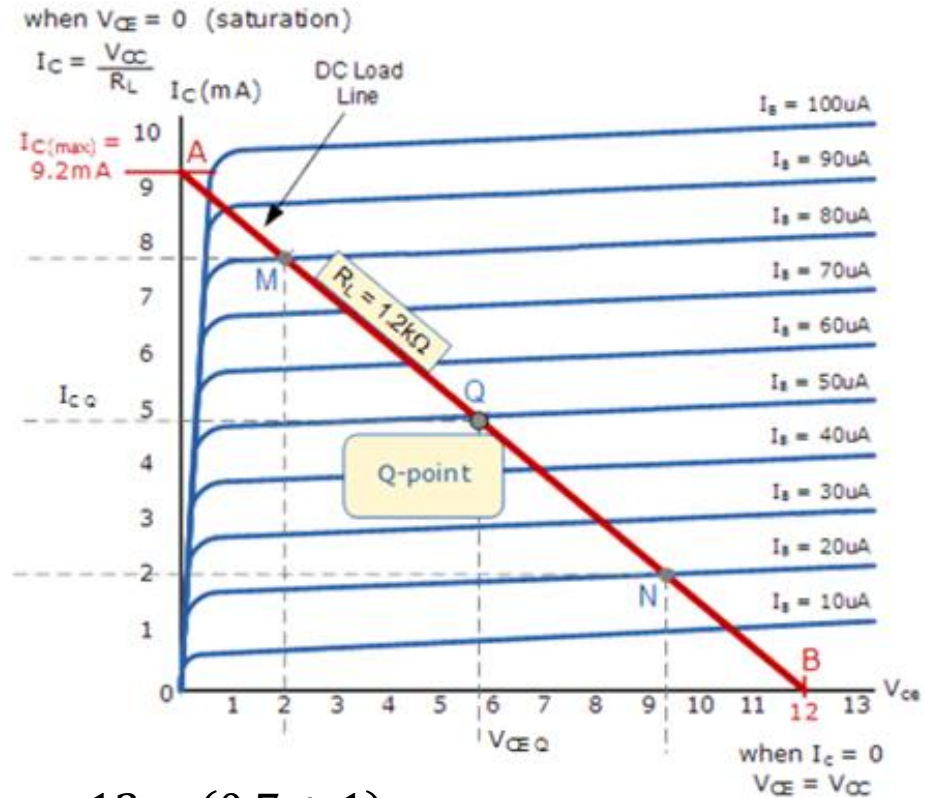
$$R_1 = \frac{V_{CC} - (V_{BE} + V_{RE})}{11I_B} = \frac{12 - (0.7 + 1)}{11 * 45,8 * 10^{-6}} = 20,45 \text{ k}\Omega$$



Common Emitter Amplifier

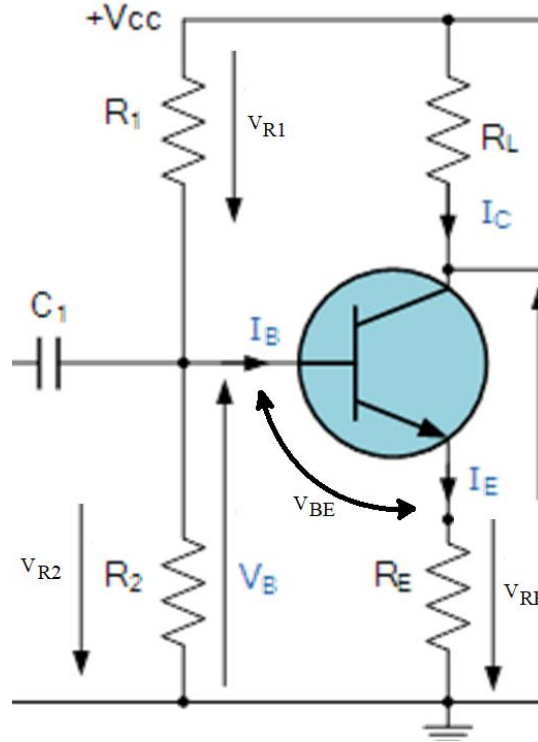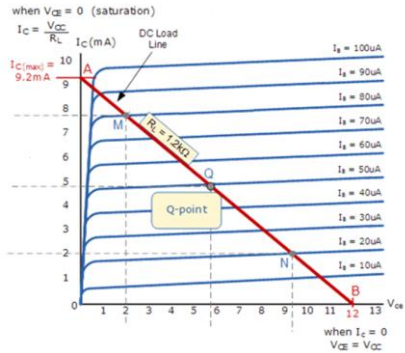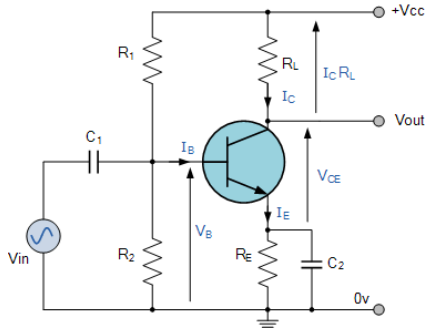


$$R_E = \frac{V_{RE}}{I_{RE}}$$

$$R_E = \frac{V_{RE}}{I_E}$$


$$I_E = I_C + I_B$$

$$R_E = \frac{1}{4.58 \times 10^{-3} + 45.8 \times 10^{-6}} = 216 \Omega$$



Common Emitter Amplifier

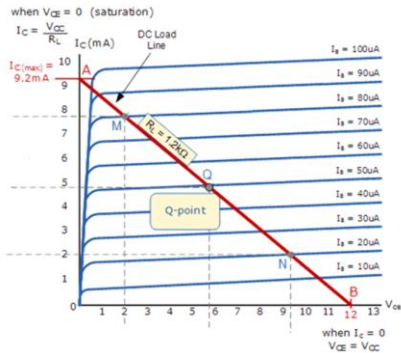


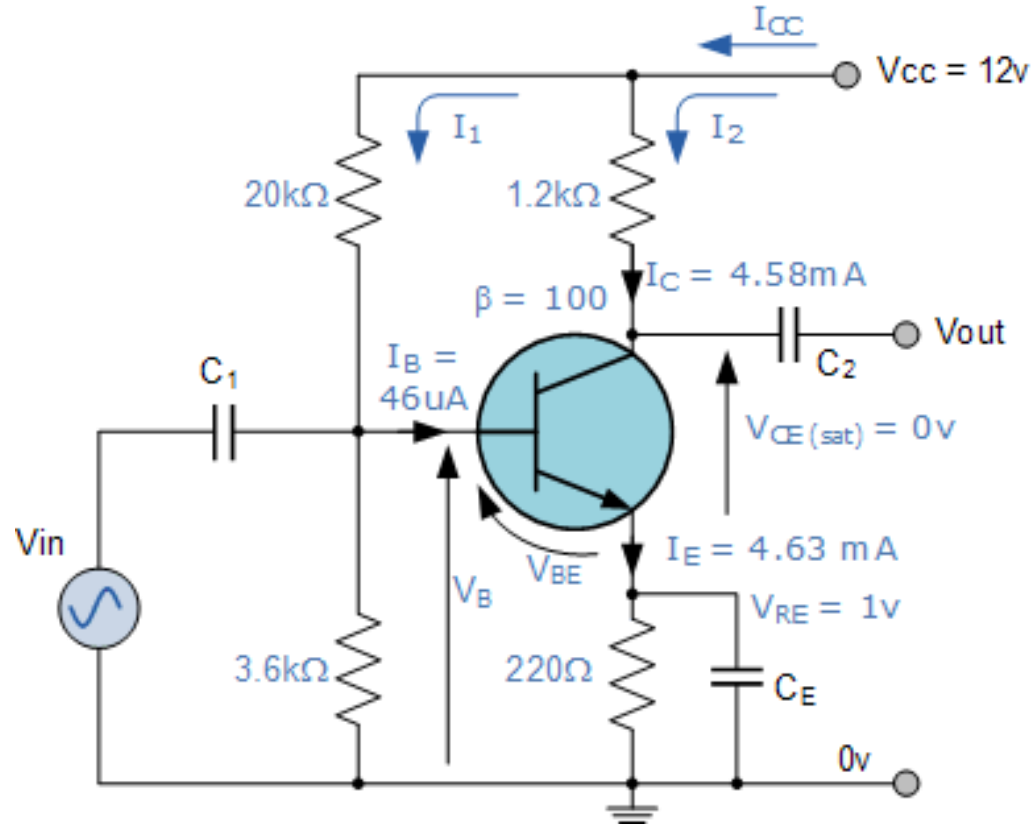
$$R_1 = 20\text{ k}\Omega$$
$$R_2 = 3.6\text{ k}\Omega$$
$$R_E = 220\text{ }\Omega$$




Capacitors in Common Emitter Amplifier

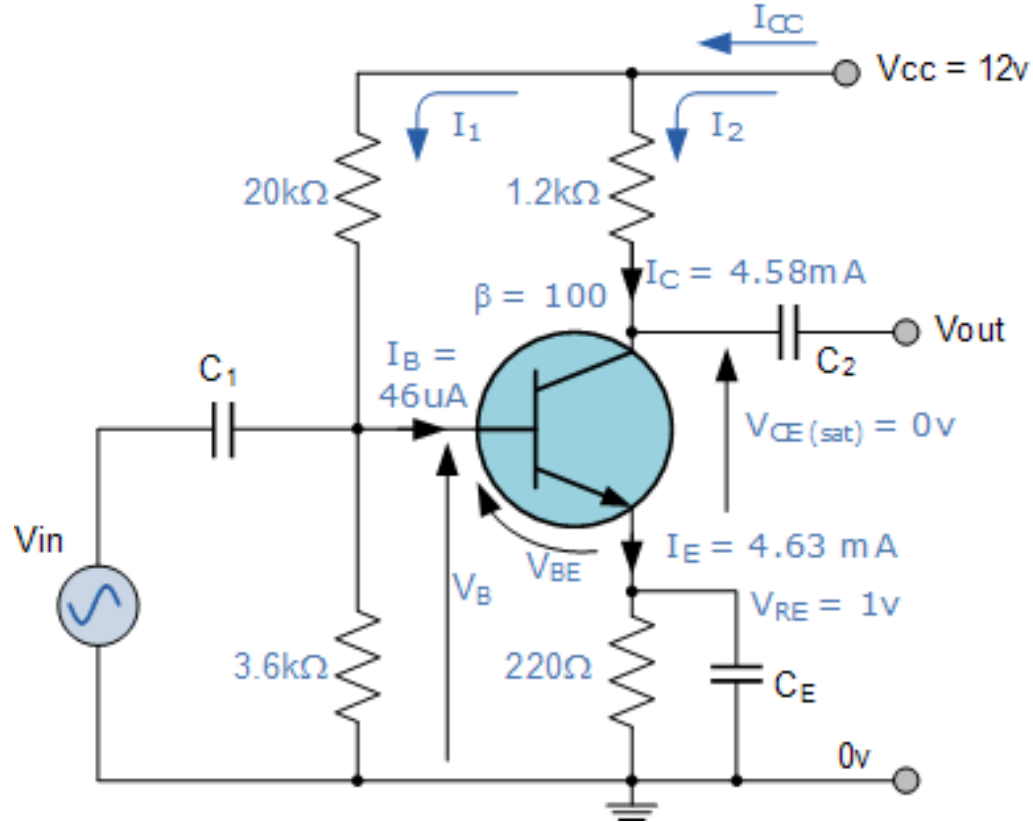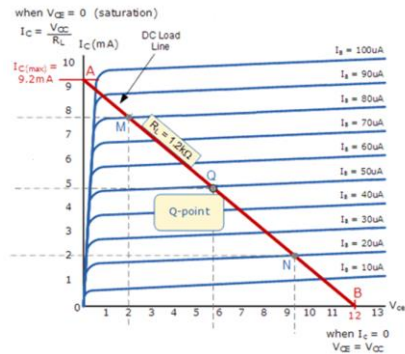



Common Emitter Amplifier

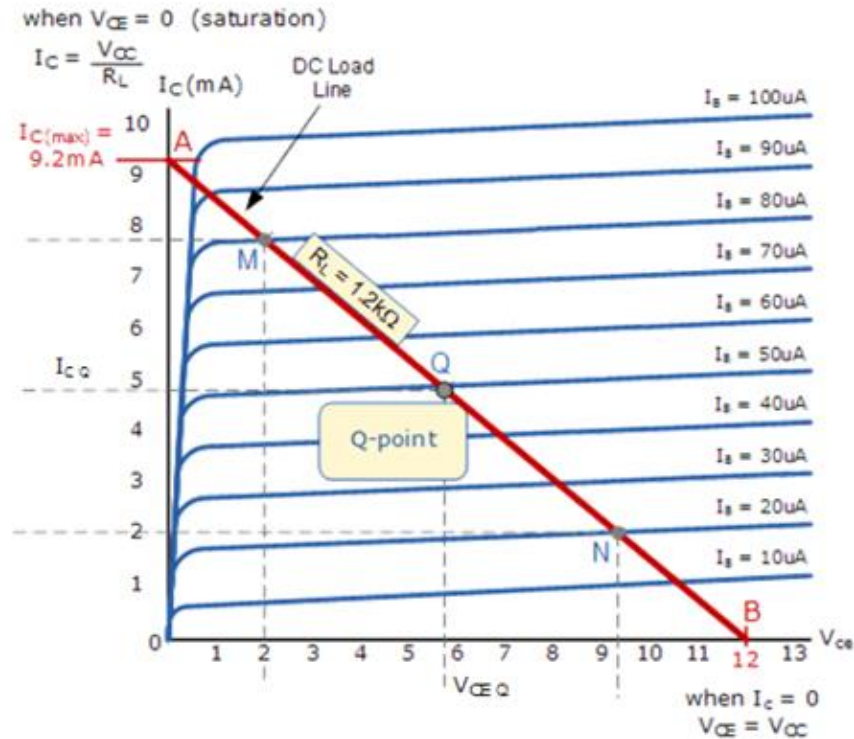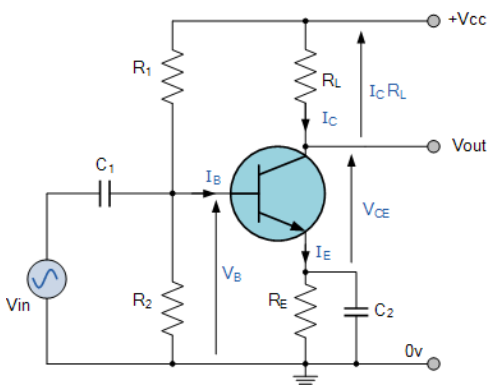

Common Emitter Amplifier

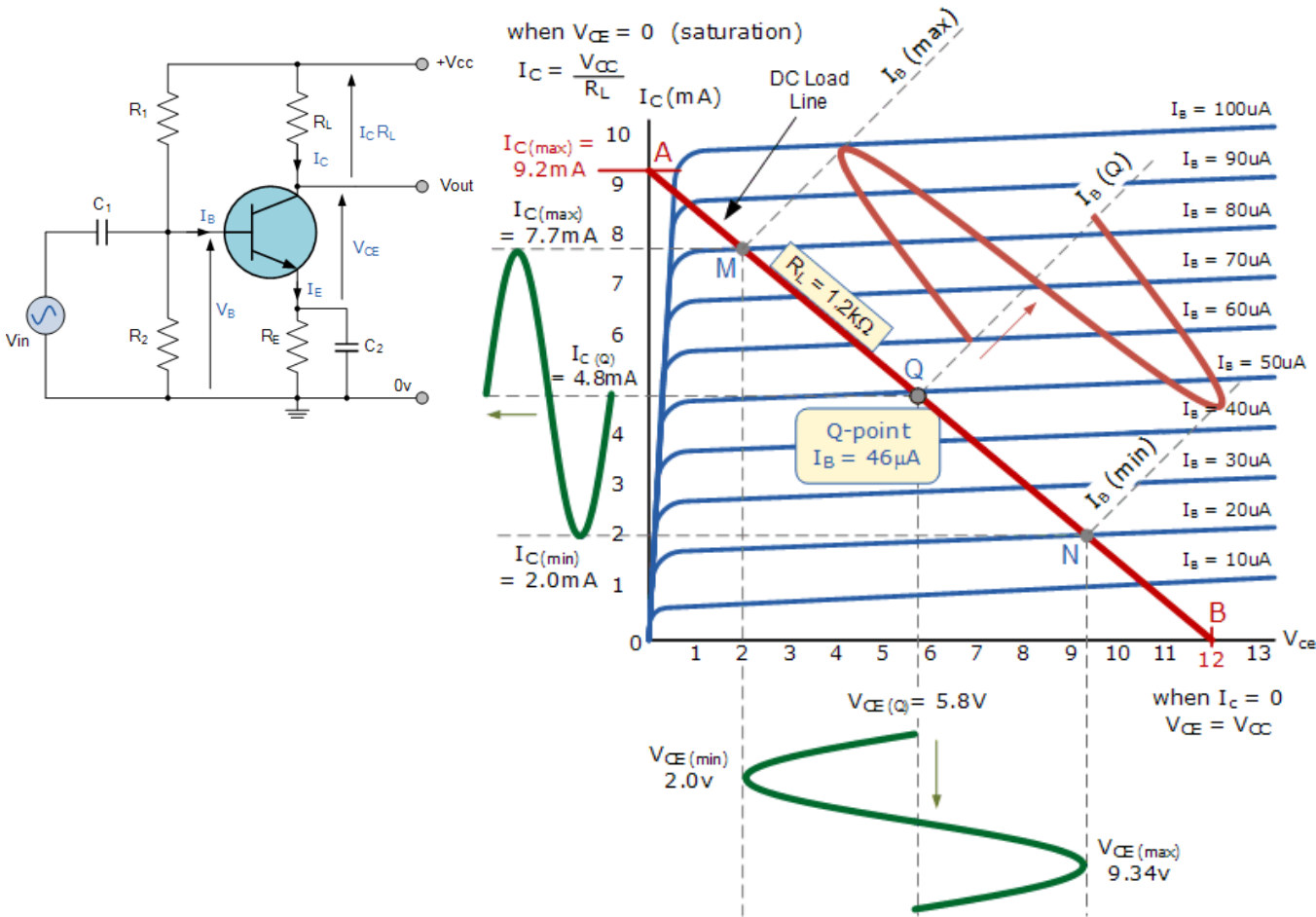

Common Emitter Amplifier

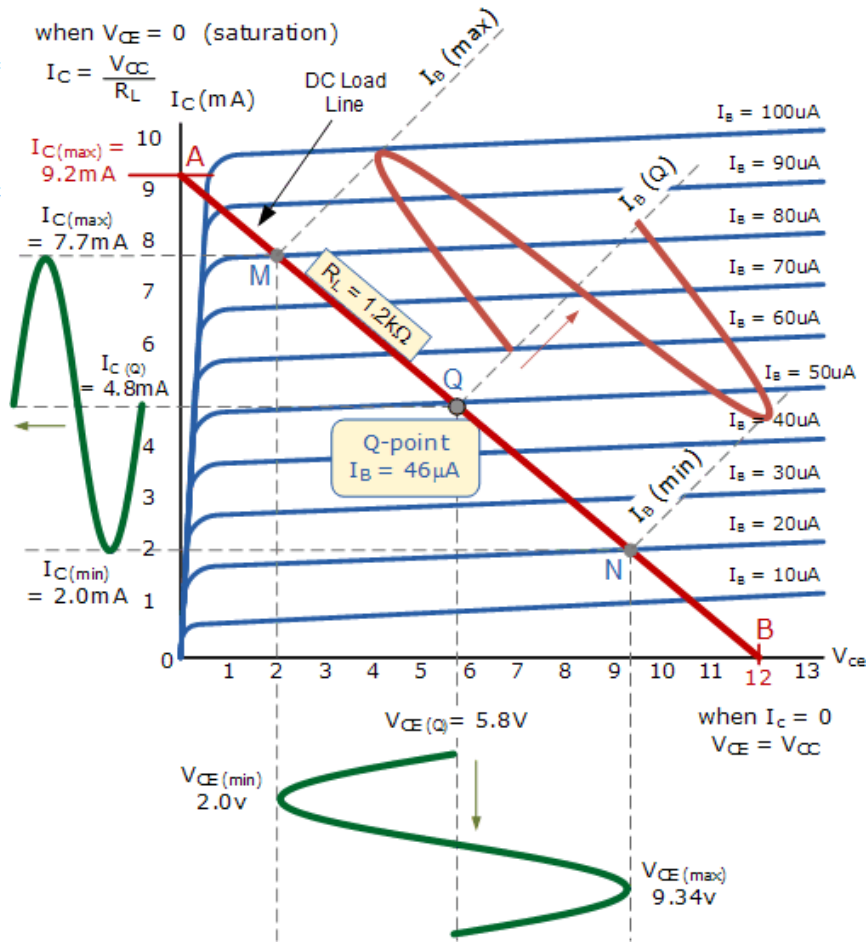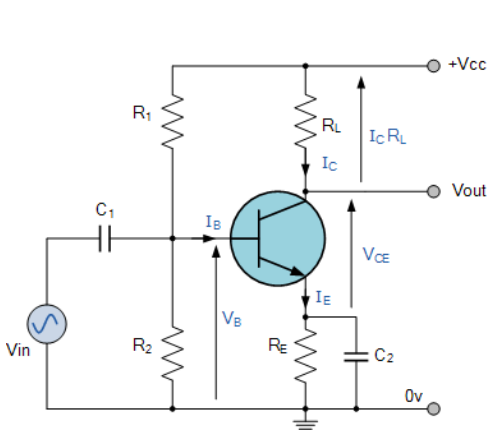



Common Emitter Voltage Gain

$$A_v = \frac{V_{OUT}}{V_{IN}} = \frac{\Delta V_L}{\Delta V_B}$$

also

$$A_v = \frac{V_{OUT}}{V_{IN}} = -\frac{R_L}{R_E}$$

Common Emitter Amplifier

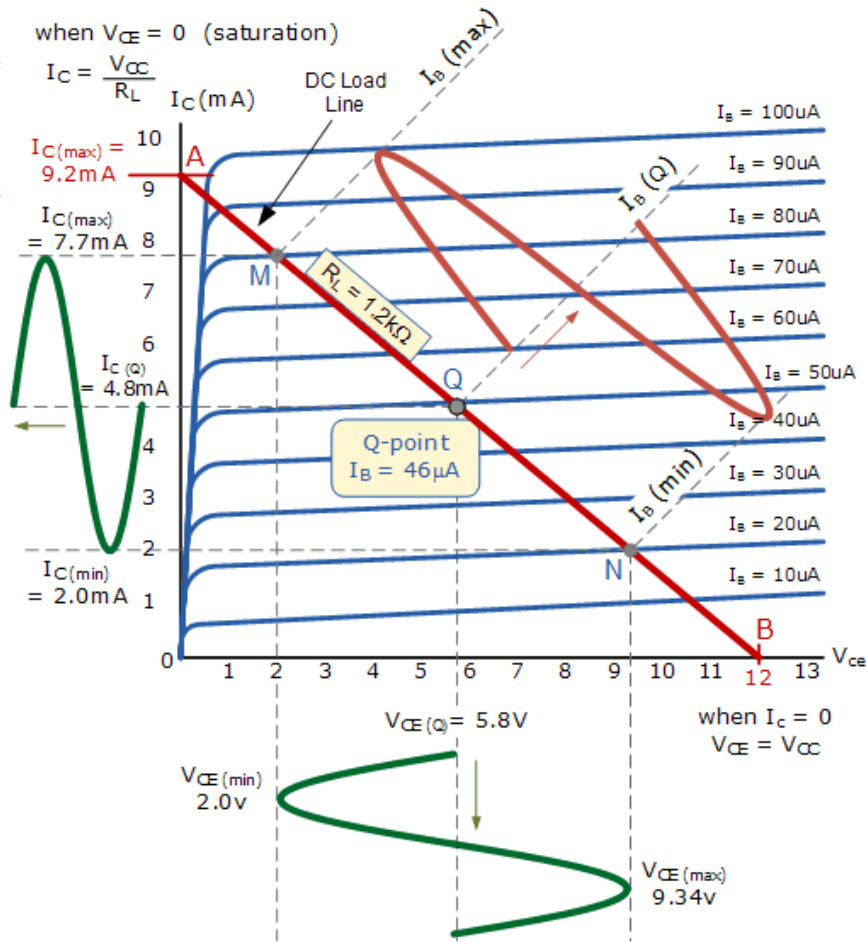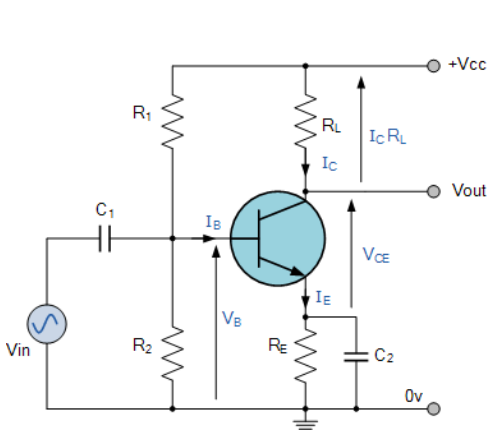

Common Emitter Voltage Gain

$$A_v = -\frac{R_L}{(R_E + r_e)}$$

$$r_e = \frac{25\text{ mV}}{I_E}$$

Gain at Low Frequencies

$$A_v = -\frac{1200}{(220 + 5.5)} = -5.32$$


Gain at High Frequencies

$$A_v = -\frac{1200}{5.5} = -218$$




iTMO


Common Source JFET Amplifier

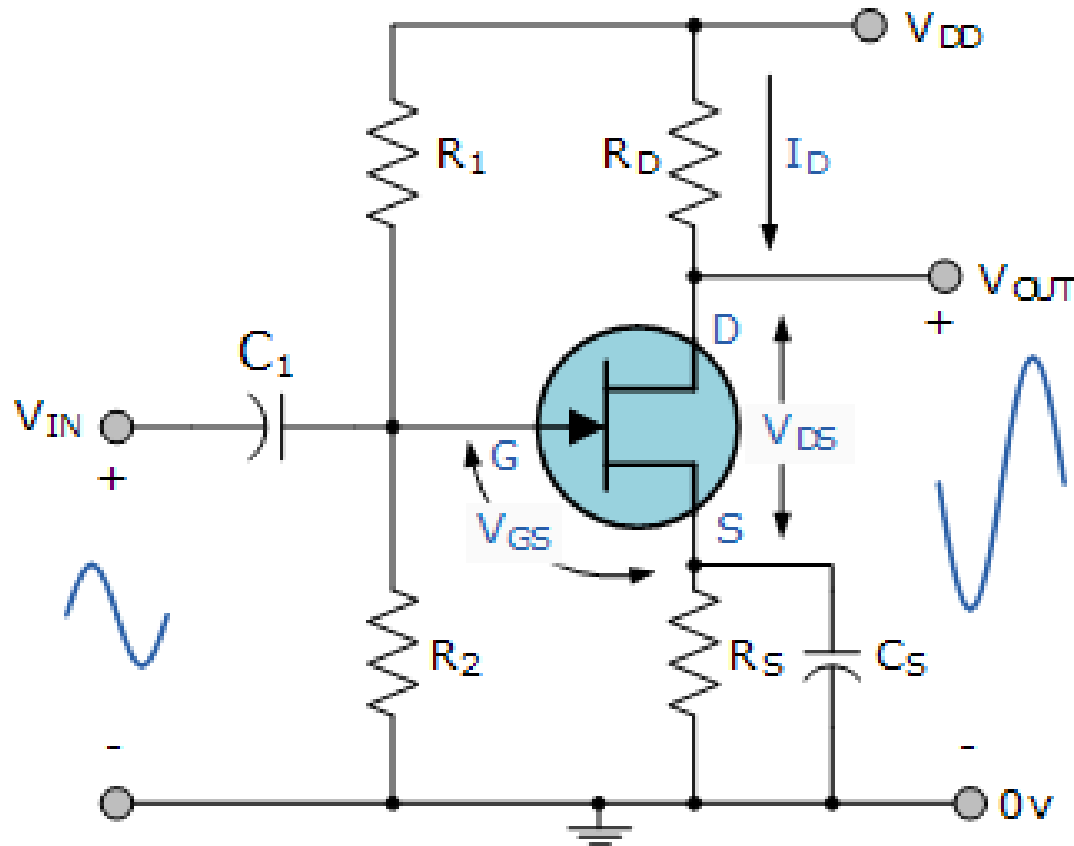


Common Source JFET Amplifier

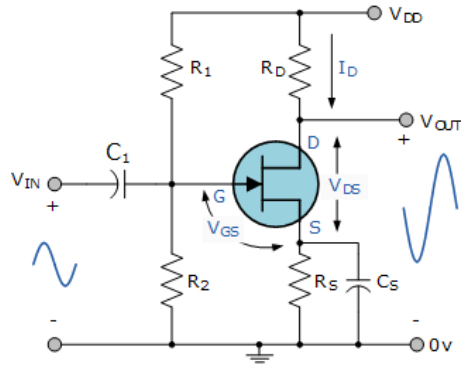


Junction FET	Bipolar Transistor
Gate (G)	Base (B)
Drain (D)	Collector (C)
Source (S)	Emitter (E)
Gate Supply (V_G)	Base Supply (V_B)
Drain Supply (V_{DD})	Collector Supply (V_{CC})
Drain Current (I_D)	Collector Current (I_C)

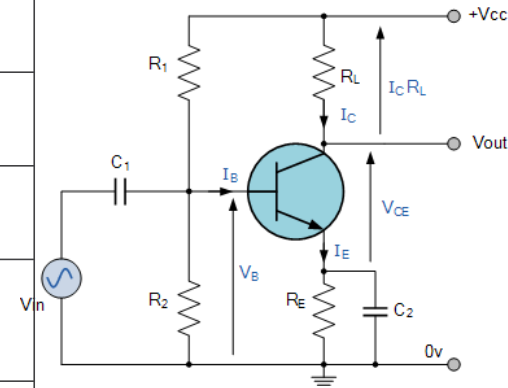

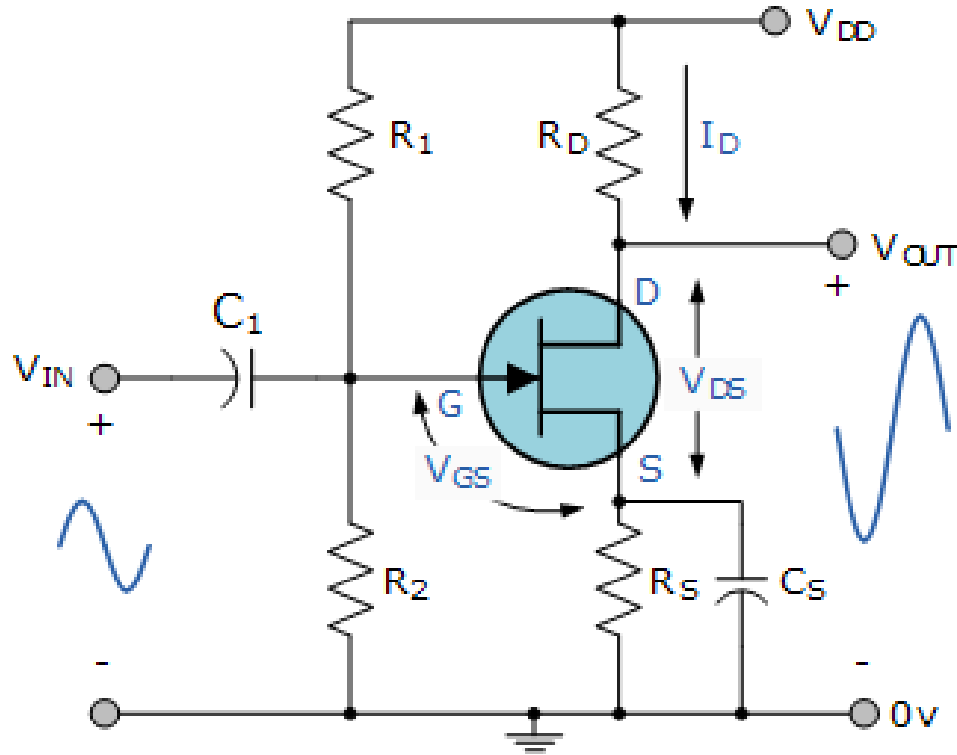

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2}$$

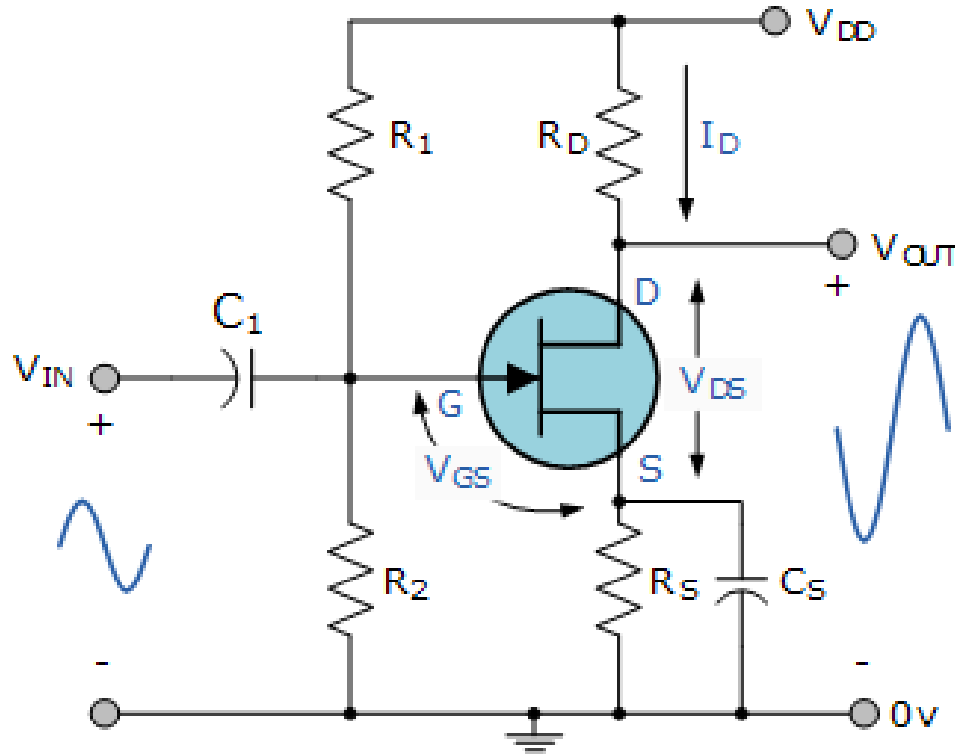

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2}$$

to keep the gate-source junction reverse biased:

$$V_G > V_S$$


Source voltage

$$V_S = V_G - V_{GS} = I_D * R_S$$

Drain current

$$I_D = \frac{V_S}{R_S} = \frac{V_{DD}}{R_D + R_S}$$


Common Source JFET Amplifier

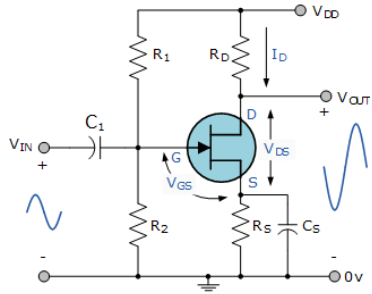


Load line $V_{DD} = V_{DS} + I_D(R_L + R_S)$

Ohmic region (A)
$$I_{Dmax} = \frac{V_{DD}}{(R_L + R_S)}$$

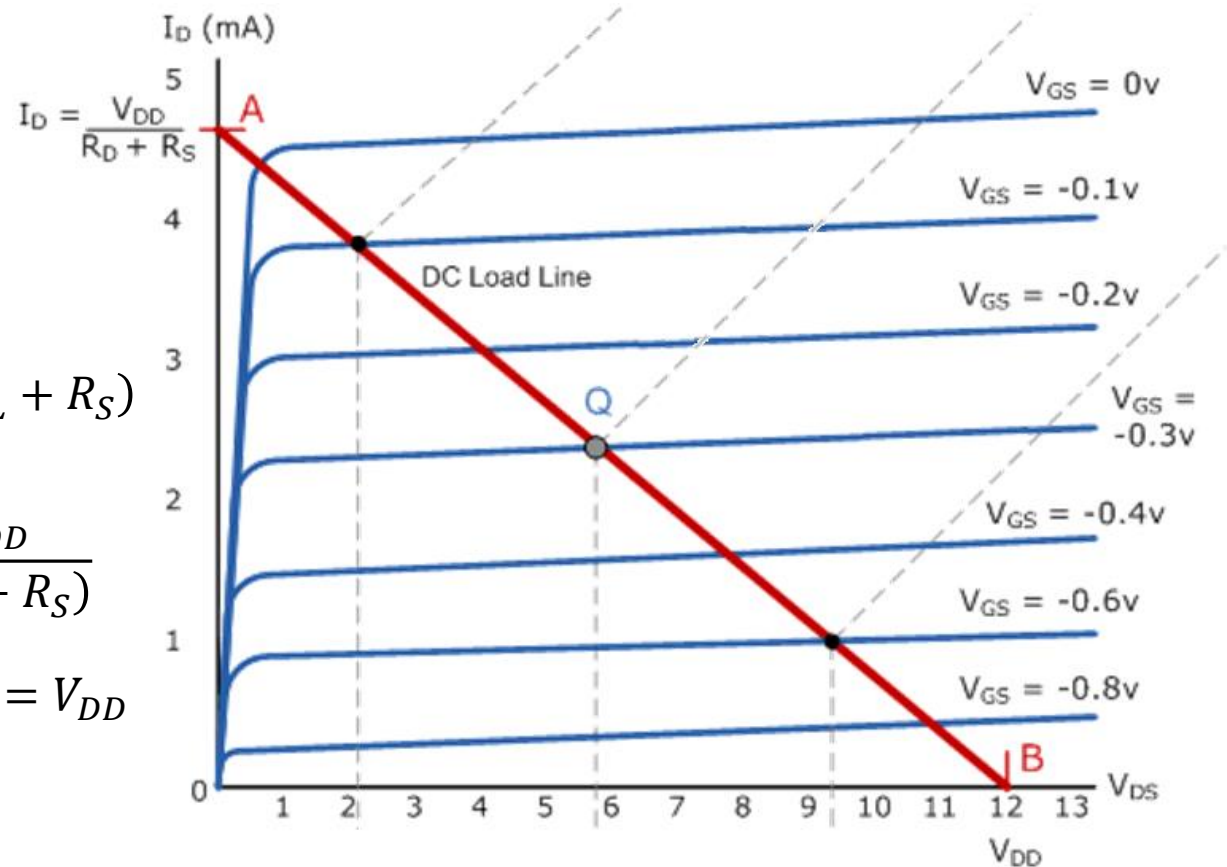Cut-off (B) $I_D = 0, \Rightarrow V_{DS} = V_{DD}$




Common Source JFET Amplifier

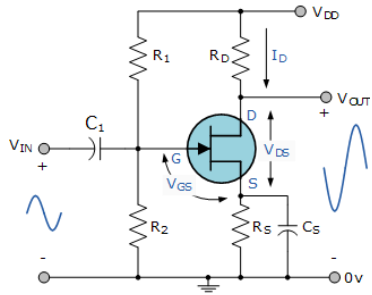


Q-point

$$V_{DSQ} \sim \frac{V_{DD}}{2}$$

$$I_{DQ} \sim \frac{I_{Dmax}}{2}$$

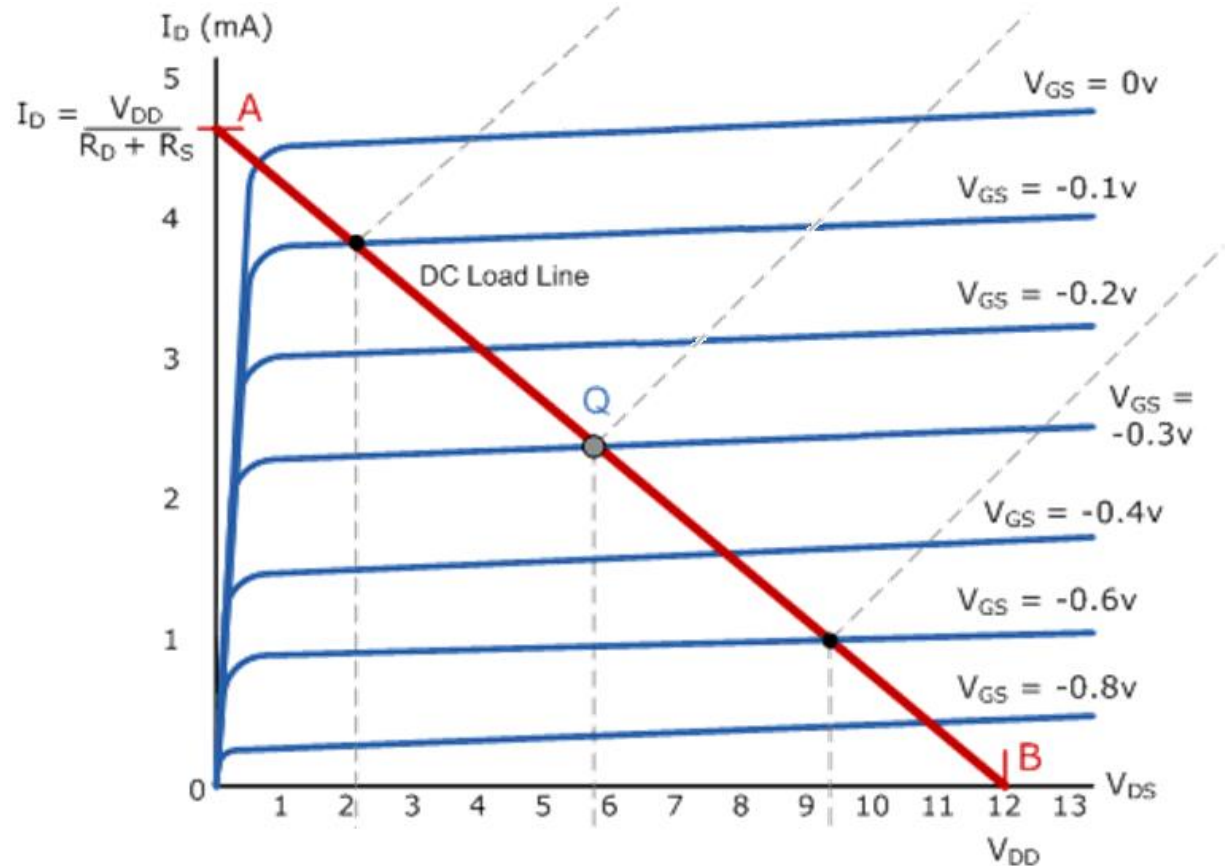


Common Source JFET Amplifier

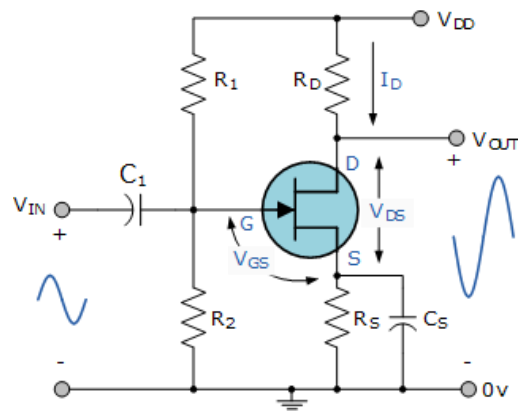

$$A_{v1} = \frac{-g_m r_o R_F}{r_o + R_F}$$

$$A_i = \frac{-g_m r_o R_F R_{in}}{R_L (r_o + R_F)} = \frac{R_{in}}{R_L} A_{v1}$$

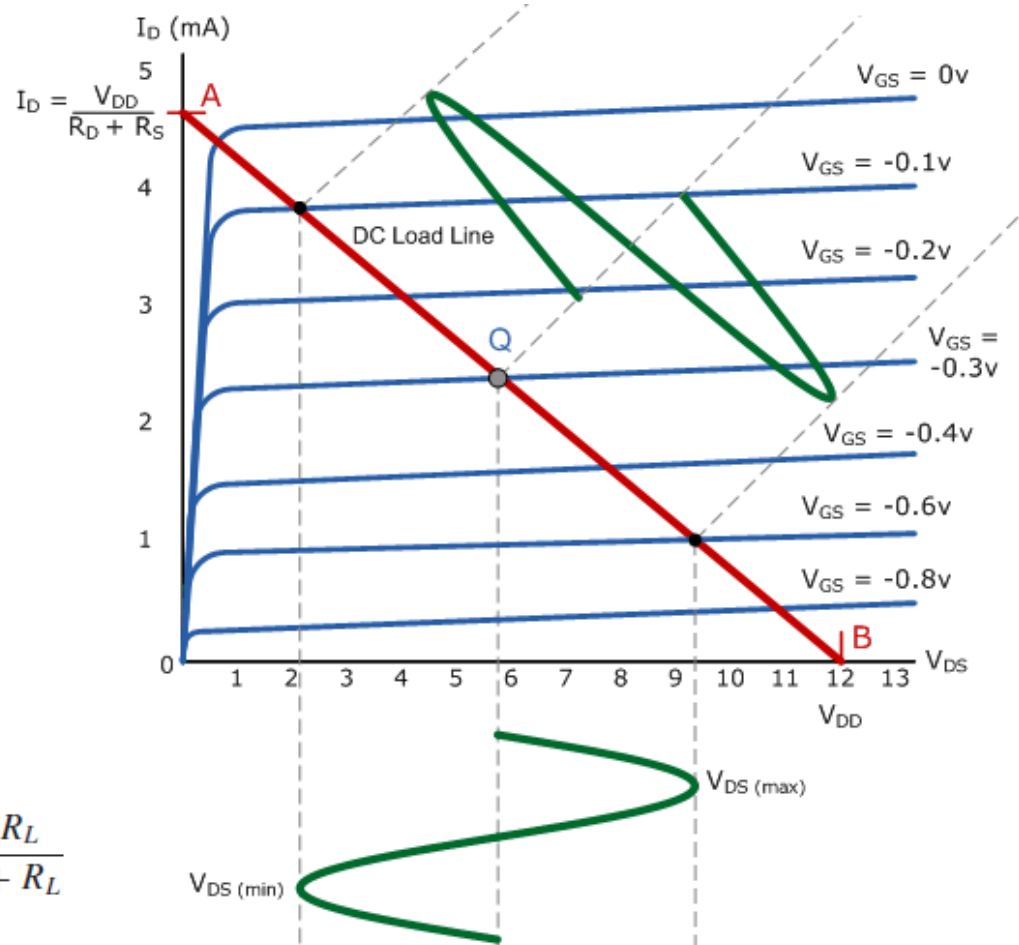where $R_F = R_D \parallel R_L = \frac{R_D R_L}{R_D + R_L}$






The background features a dark gray grid pattern. In the top right and bottom left corners, there are wavy, glowing purple lines that create a sense of motion or energy.




iTMO

Frequency Response




Typical Frequency Response

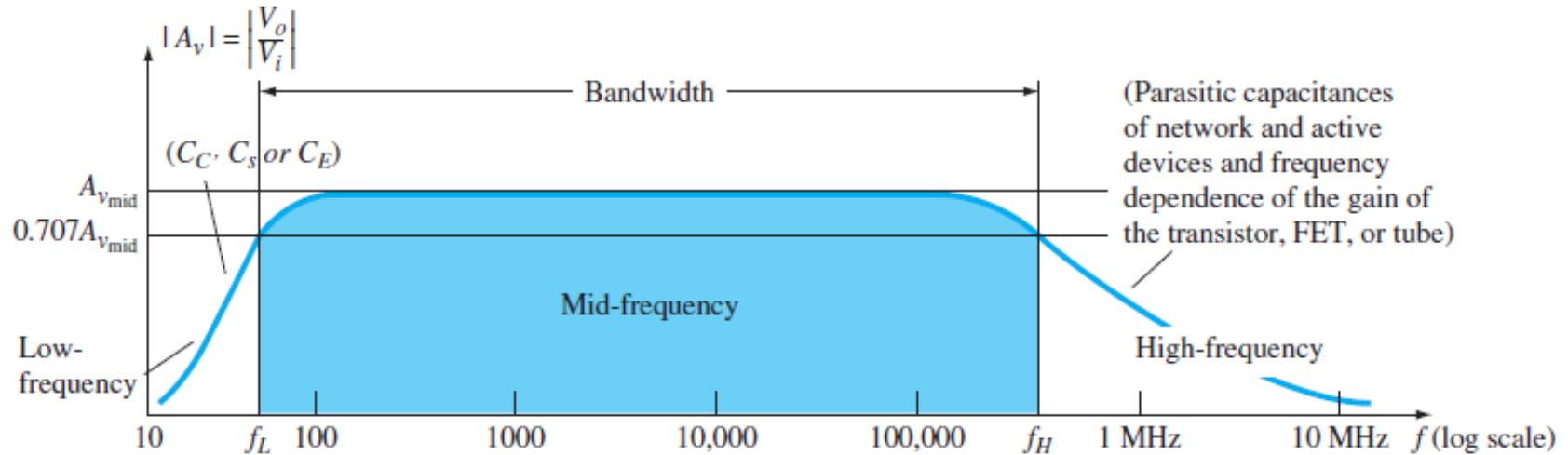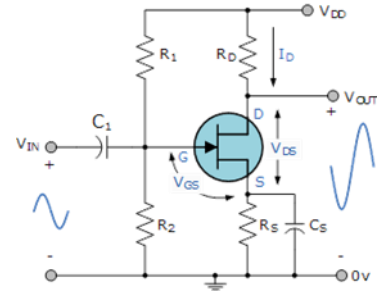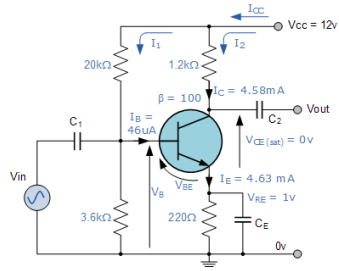


Typical Frequency Response

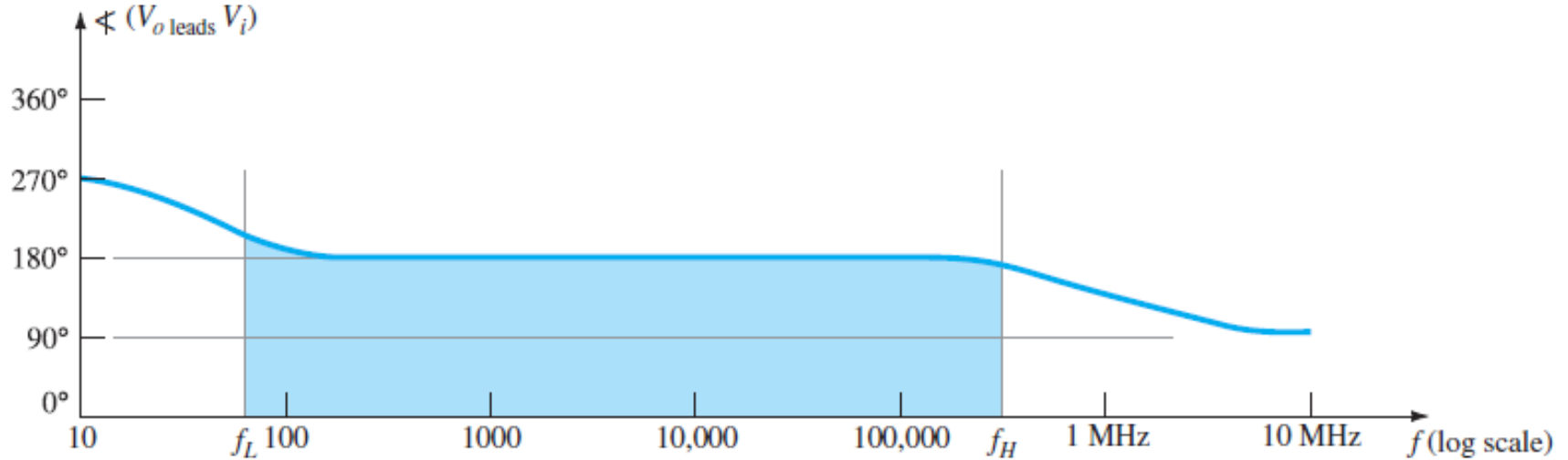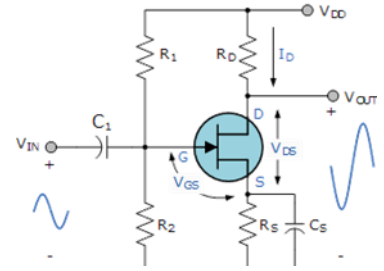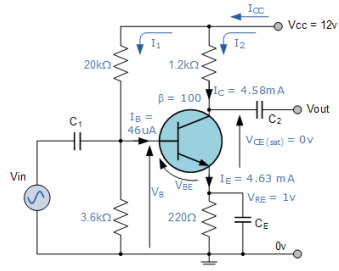


Typical Frequency Response

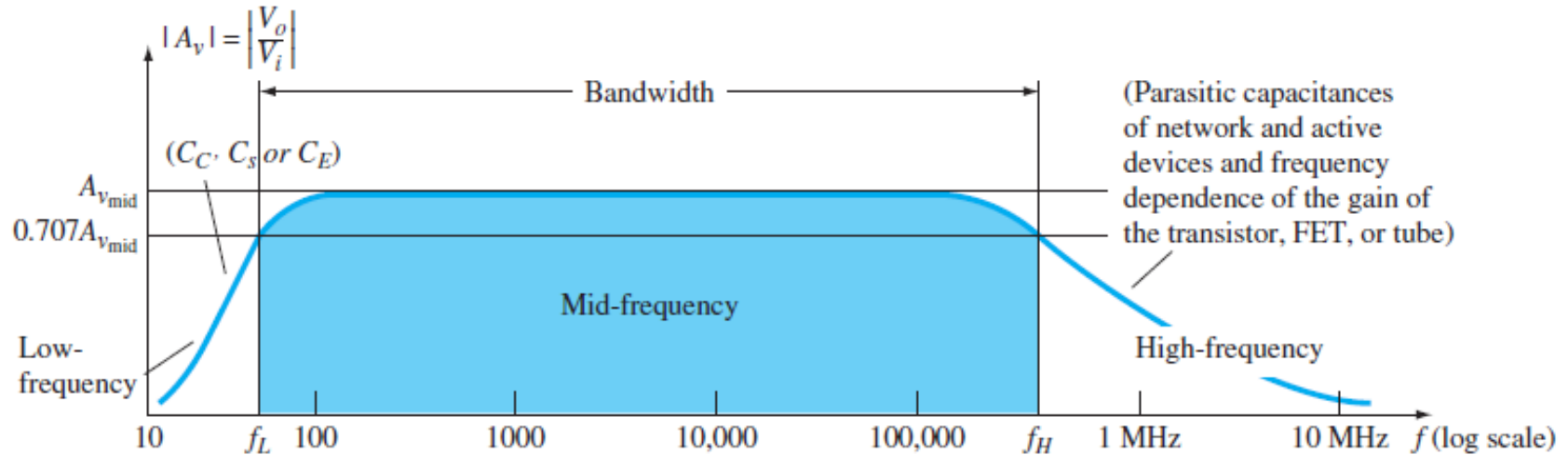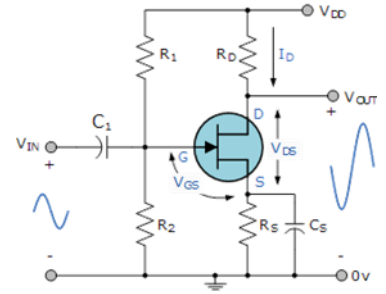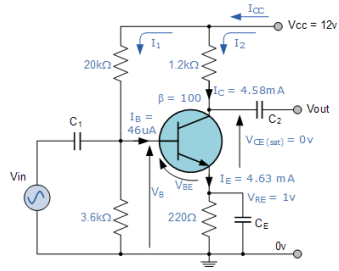

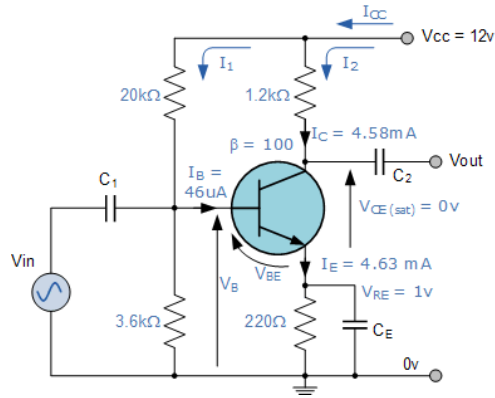


RC circuit

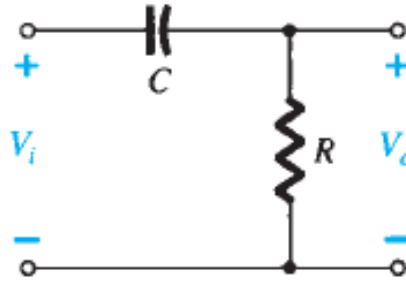

$$V_o = \frac{RV_i}{R + X_C}$$


$$C = \frac{1}{2\pi f_L R}$$

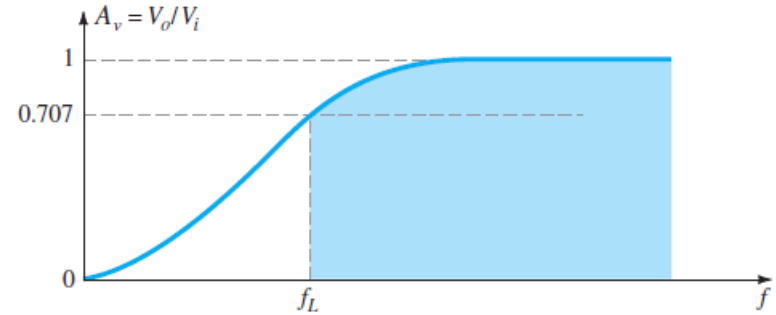Low-frequency response for the RC circuit




$$|A_v| = \frac{V_o}{V_i} = \frac{1}{\sqrt{2}} = 0.707 \big|_{X_C=R}$$

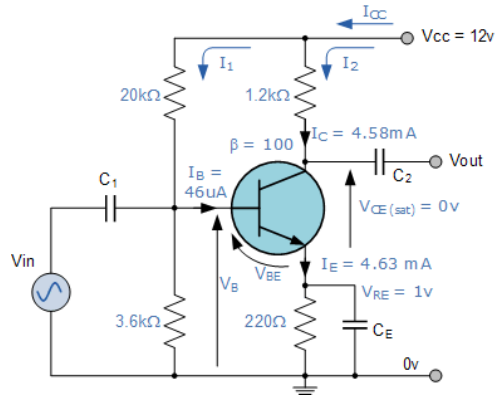Where R is equivalent resistor of input or output circuit, or R_E or R_S 45




Miller effect input capacitance

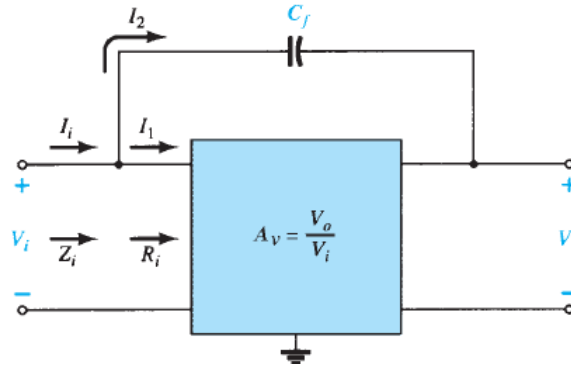

$$C_{M_i} = (1 - A_v)C_f$$

Miller output capacitance


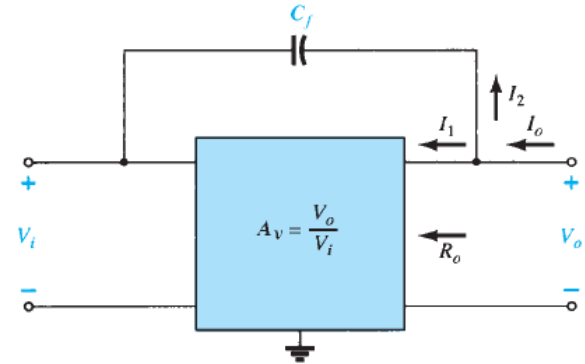


$$C_{M_o} = \left(1 - \frac{1}{A_v}\right)C_f$$

For the usual situation
where $A_v \gg 1$

$$C_{M_o} \cong C_f$$


Hi frequency

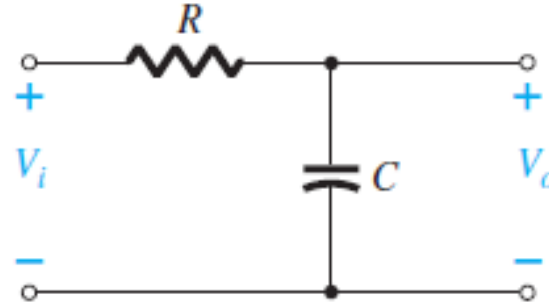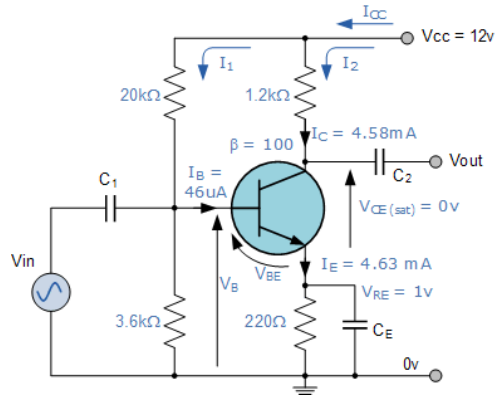

$$f_{Hi} = \frac{1}{2\pi R_{eq} C_{eq}}$$

Where R_{eq} , C_{eq} is equivalent resistor and capacitance of input or output circuit

Parasitic capacitances

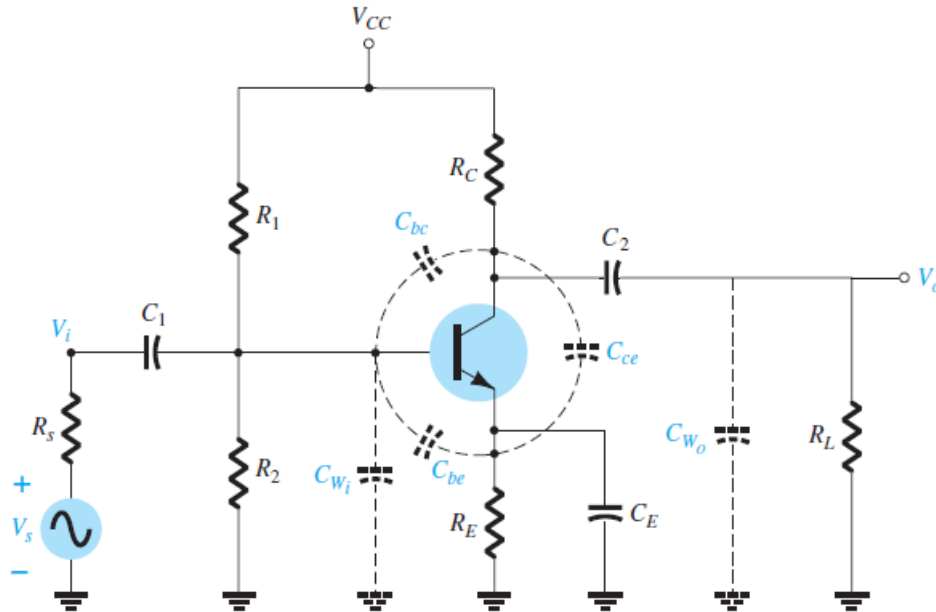

h_{fe} (or β) Variation

$$h_{fe} = \frac{h_{fe \text{ mid}}}{1 + j \left(f / f_{\beta} \right)}$$

where

$$f_{\beta} = \frac{1}{h_{fe \text{ mid}}} \frac{1}{2\pi r_e (C_{BE} + C_{BC})}$$

Equation clearly reveals that because r_e is a function of the network design: f_{β} is a function of the bias configuration.

$$h_{fe} = \frac{h_{fe\ mid}}{1 + j\left(f/f_{\beta}\right)}$$

direct conversion for
determining f_{β}

if f_{α} and α are specified


$$f_{\beta} = f_{\alpha}(1 - \alpha)$$


Gain-Bandwidth Product


$$GBP = A_{v\ mid} * \Delta f$$

$$\text{At } A_v = 1, \Delta f = f_T$$

$$f_T = A_{v\ mid} * f_H$$

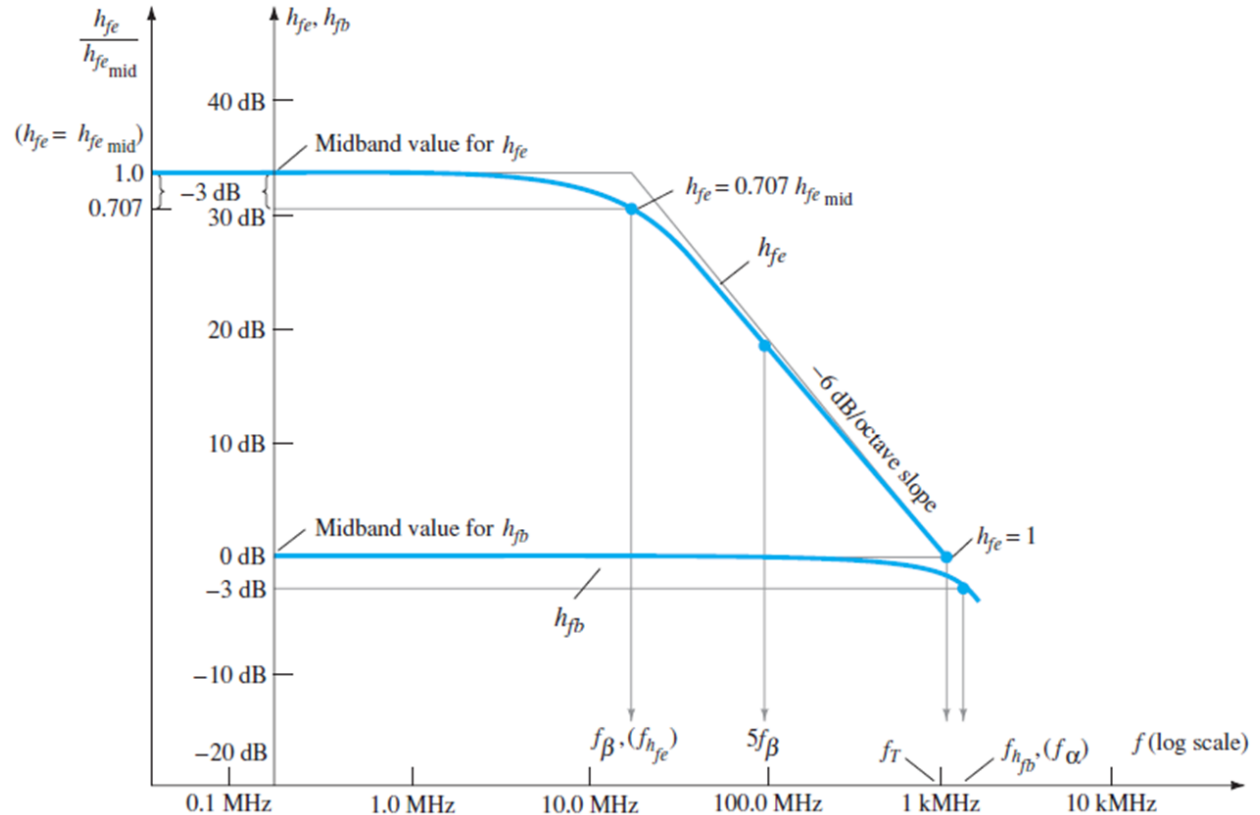


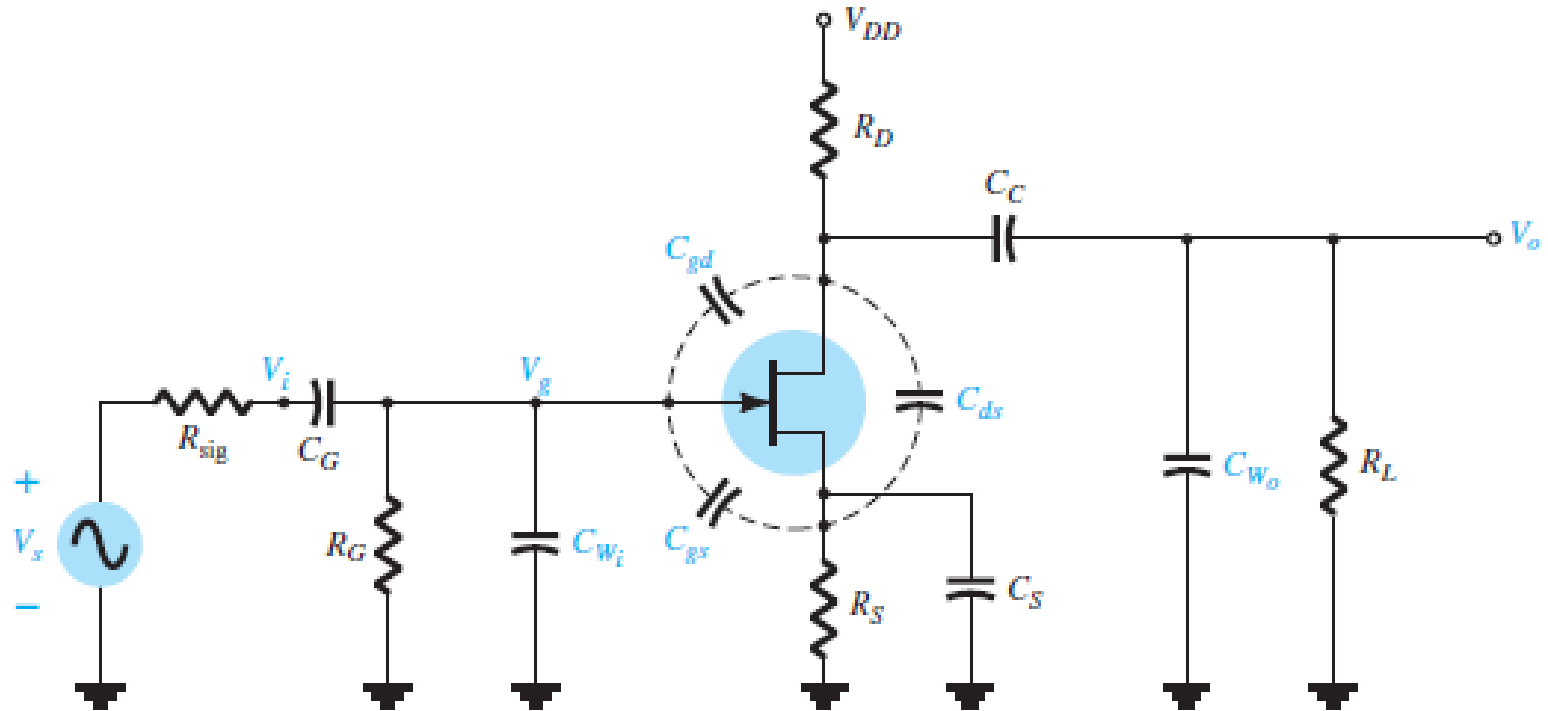

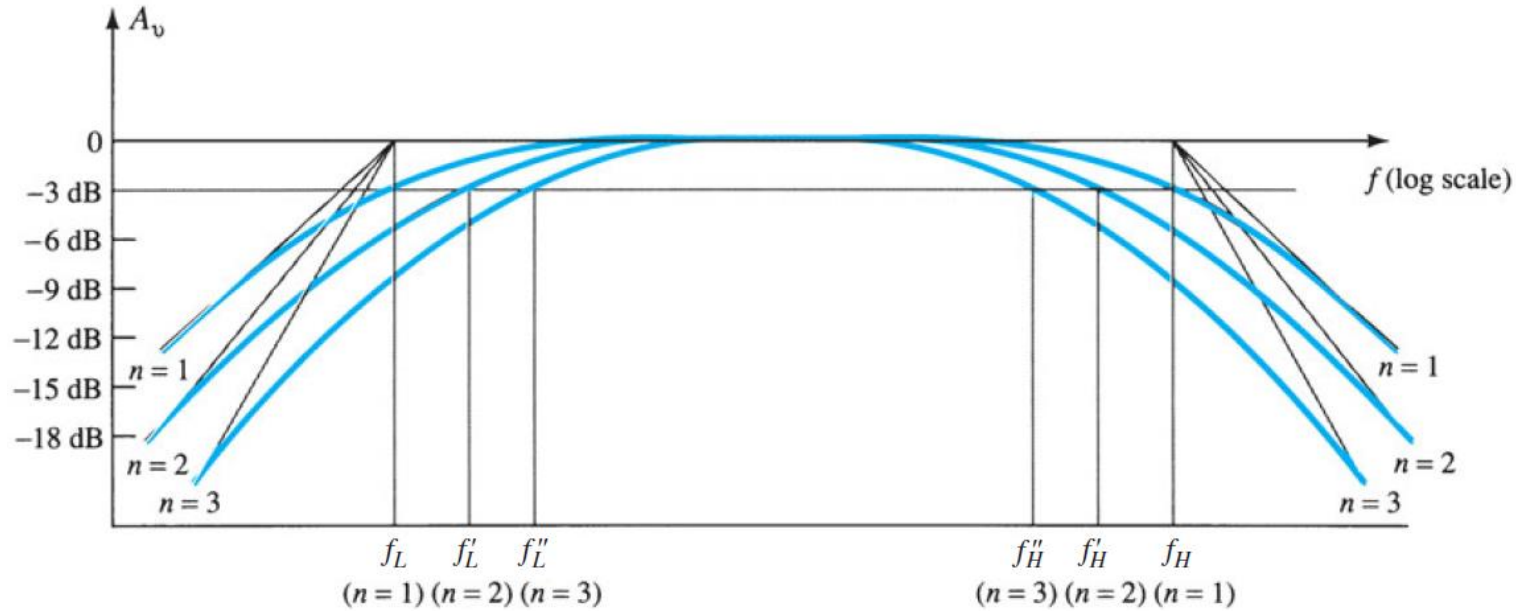

if all the cascades are the same, then
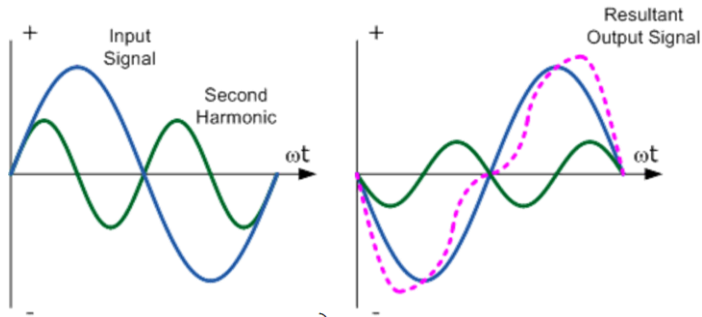
$$f'_L = \frac{f_L}{\sqrt{2^{1/n} - 1}} \quad f'_H = (\sqrt{2^{1/n} - 1})f_H$$




Harmonic distortion can be defined as


$$\% nth \text{ harmonic distortion} = \% D_n = \frac{|A_n|}{|A_1|} \times 100\%$$

The fundamental component is typically larger than any harmonic component.

Total Harmonic Distortion
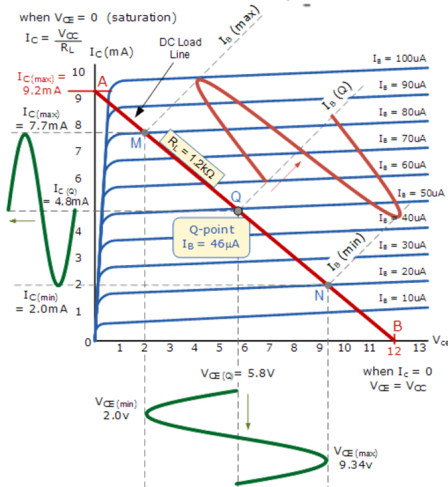
$$\% THD = \sqrt{D_2^2 + D_3^2 + D_4^2 + \dots} \times 100\%$$



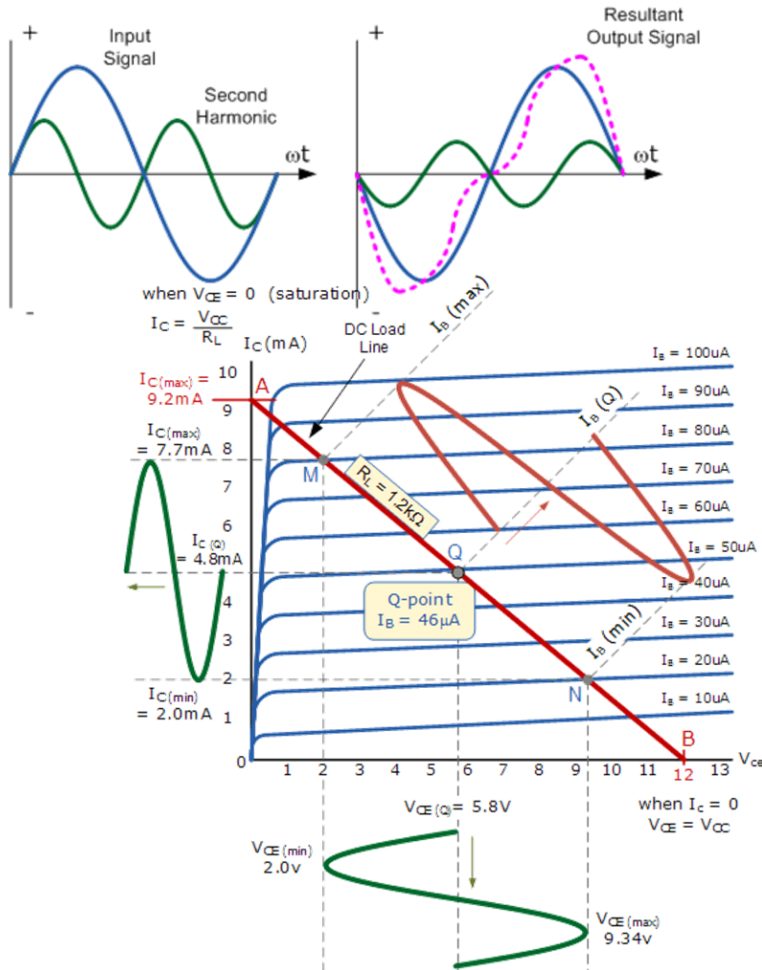

the second harmonic distortion in terms of measured collector current

$$D_2 = \left| \frac{\frac{1}{2}(I_{C_{max}} + I_{C_{min}}) - I_{C_Q}}{I_{C_{max}} - I_{C_{min}}} \right| \times 100\%$$

the second harmonic distortion in terms of measured collector-emitter voltages

$$D_2 = \left| \frac{\frac{1}{2}(V_{CE_{max}} + V_{CE_{min}}) - V_{CE_Q}}{V_{CE_{max}} - V_{CE_{min}}} \right| \times 100\%$$

1. Sarma M. S. Introduction to electrical engineering. – New York : Oxford University Press, 2001. – C. 715-716.
2. Boylestad, Robert L. Electronic devices and circuit theory / Robert L. Boylestad, Louis Nashelsky.—11th ed.
3. ISBN 978-0-13-262226-4 Scherz P., Monk S. Practical electronics for inventors. – McGraw-Hill Education, 2016.
4. Horowitz, Paul, and Winfield Hill. "The Art of Electronics. 3rd." *New York, NY, USA: University of Cambridge* (2015).
5. All about circuits (<https://www.allaboutcircuits.com/>)
6. <https://www.electronics-tutorials.ws/>
7. <https://en.wikipedia.org/>

The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a bright purple color, creating a modern, tech-oriented aesthetic.

iTMO

Thank you for your attention!

The background features a dark gray grid pattern. In the top right and bottom left corners, there are decorative wavy lines in a vibrant purple color, creating a modern, abstract aesthetic.

iTMO

Amplifier configurations